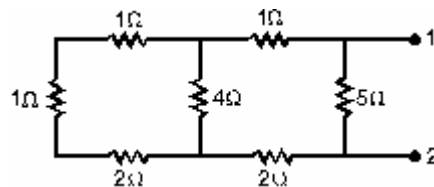


1. A portion of a circuit is shown, with the values of the currents given for some branches. What is the direction and value of the current i ?




- A) \downarrow , 6A
 B) \uparrow , 6A
 C) \downarrow , 4A
 D) \uparrow , 4A
 E) \downarrow , 2A
2. A total resistance of 3.0Ω is to be produced by combining an unknown resistor R with a 12Ω resistor. What is the value of R and how is it to be connected to the 12Ω resistor?
- A) 4.0Ω , parallel
 B) 4.0Ω , series
 C) 2.4Ω , parallel
 D) 2.4Ω , series
 E) 9.0Ω , series
3. Nine identical wires, each of diameter d and length L , are connected in parallel. The combination has the same resistance as a single similar wire of length L but whose diameter is:
- A) $3d$
 B) $9d$
 C) $d/3$
 D) $d/9$
 E) $d/81$
4. The equivalent resistance between points 1 and 2 of the circuit shown is:



- A) 4Ω
 B) 4.5Ω
 C) 6Ω
 D) 3Ω
 E) 2.5Ω

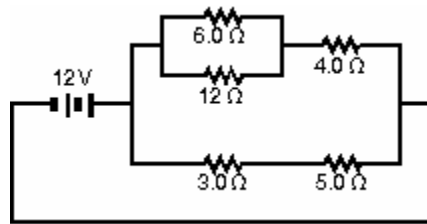5. The current in the $5.0\text{-}\Omega$ resistor in the circuit shown is:



- A) $0.42\ \text{A}$
B) $0.67\ \text{A}$
C) $1.5\ \text{A}$
D) $2.4\ \text{A}$
E) $3.0\ \text{A}$
6. A $2\text{-}\Omega$ resistor and a $4\text{-}\Omega$ resistor are connected in parallel to a 6-V battery. The rate of thermal energy dissipated by the $2\text{-}\Omega$ resistor is:
- A) $8\ \text{W}$
B) $6\ \text{W}$
C) $9\ \text{W}$
D) $18\ \text{W}$
E) none of these

Answer Key --

1. A
2. A
3. A
4. E
5. C
6. D