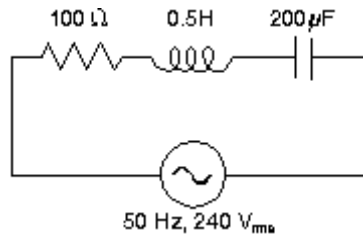


1. A charged capacitor and an inductor are connected in series. At time $t = 0$ the current is zero, but the capacitor is charged. If T is the period of the resulting oscillations, the next time, after $t = 0$ that the energy stored in the electric field of the capacitor is a maximum is:
 - A) T
 - B) $T/4$
 - C) $T/2$
 - D) T
 - E) $2T$
2. We desire to make an LC circuit that oscillates at 100 Hz using an inductance of 2.5 H. We also need a capacitance of:
 - A) 1 F
 - B) 1 mF
 - C) 1 μF
 - D) 100 μF
 - E) 1 pF
3. An RLC circuit is driven by an alternative voltage source $E = 162.6 \sin(377t)$ volt. The frequency and the amplitude of this voltage source are:
 - A) 50 Hz, 162.6 volt
 - B) 60 Hz, 162.6 volt
 - C) 50 Hz, 115 volt
 - D) 60 Hz, 115 volt
 - E) 377 Hz, 162.6 volt
4. An LC circuit has a capacitance of 12 μF and an inductance of 25 mH with a resistance of 6.0 Ω . The circuit oscillates with an angular frequency of:
 - A) 1.2×10^3 rad/s
 - B) 1.4×10^3 rad/s
 - C) 1.8×10^3 rad/s
 - D) 2.2×10^3 rad/s
 - E) 2.6×10^3 rad/s
5. In a purely inductive circuit, the current lags the voltage by:
 - A) 1/4 cycle
 - B) 1/2 cycle
 - C) 3/4 cycle
 - D) 1 cycle
 - E) an amount that depends on the frequency

6. When the amplitude of the alternating emf source in a series RLC circuit is doubled:
- the impedance is doubled
 - the voltage across the capacitor is halved
 - the capacitive reactance is halved
 - the power factor is doubled
 - the current amplitude is doubled
7. An RLC series circuit is connected to an oscillator with $E_m = 100$ V. If the voltage amplitudes V_R , V_L , and V_C are all equal to each other, then V_R must be:
- 33 V
 - 50 V
 - 67 V
 - 87 V
 - 100 V
8. The impedance of the circuit shown is:



- $41.1\ \Omega$
- $100\ \Omega$
- $173\ \Omega$
- $187\ \Omega$
- $241\ \Omega$

Answer Key --

- C
- C
- B
- C
- A
- E
- E
- C