

- A battery is used to charge a series combination of two identical capacitors. If the potential difference across the battery terminals is V and total charge Q flows through the battery during the charging process then the charge on the positive plate of each capacitor and the potential difference across each capacitor are:

 - $Q/2$ and $V/2$, respectively
 - Q and V , respectively
 - $Q/2$ and V , respectively
 - Q and $V/2$, respectively
 - Q and $2V$, respectively


- A $2\text{-}\mu\text{F}$ and a $1\text{-}\mu\text{F}$ capacitor are connected in parallel and a potential difference is applied across the combination. The $2\text{-}\mu\text{F}$ capacitor has:

 - twice the charge of the $1\text{-}\mu\text{F}$ capacitor
 - half the charge of the $1\text{-}\mu\text{F}$ capacitor
 - twice the potential difference of the $1\text{-}\mu\text{F}$ capacitor
 - half the potential difference of the $1\text{-}\mu\text{F}$ capacitor
 - none of the above

- Two identical capacitors, each with capacitance C , are connected in parallel and the combination is connected in series to a third identical capacitor. The equivalent capacitance of this arrangement is:

 - $2C/3$
 - C
 - $3C/2$
 - $2C$
 - $3C$

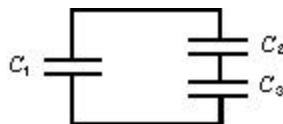- Capacitor C_1 is connected alone to a battery and charged until the magnitude of the charge on each plate is q_0 . Then it is removed from the battery and connected to two other capacitors C_2 and C_3 as shown. The final charges on the capacitors are related by:



- $q_0 = q_1 + q_2 + q_3$
- $q_1 + q_2 + q_3 = 0$
- $q_0 = q_1, q_2 + q_3 = 0$
- $q_0 = q_1 + q_2, q_2 = q_3$

E) $q_0 = q_2 + q_3, q_1 = 0$

5. A parallel-plate capacitor has a plate area of 0.2 m^2 and a plate separation of 0.1 mm . If the charge on each plate has a magnitude of $4 \times 10^{-6} \text{ C}$ the electric field between the plates is approximately:
- A) 0
 - B) $4 \times 10^2 \text{ V/m}$
 - C) $1 \times 10^6 \text{ V/m}$
 - D) $2 \times 10^6 \text{ V/m}$
 - E) $4 \times 10^{12} \text{ V/m}$

Answer Key:

- 1. D
- 2. A
- 3. A
- 4. D
- 5. D