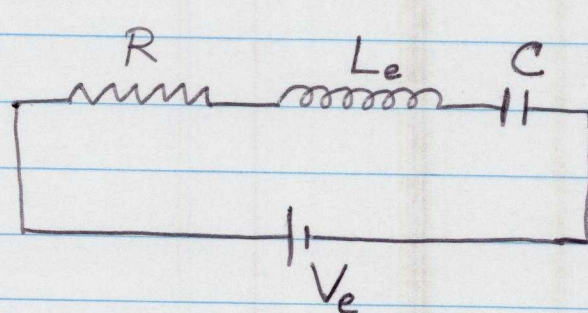


Identify the analogy of the principle

E2-12

$$\delta \int L dt = 0 \quad \text{for electrical}$$

circuits. Consider the circuit shown



$L_e \equiv$  inductance  
here

$C \equiv$  capacitance

$R \equiv$  resistance

$V_e \equiv$  emf of battery.

We want  $V_e = IR + L\dot{I} + \frac{q}{C}$

$I \equiv \dot{q}$ ,  $q(t)$  is the charge flowing through the circuit at time  $t$ ,

$$\therefore \text{we need } L\ddot{q} + \frac{q}{C} - V_e = -R\dot{q}$$

$$= \frac{d}{dt}(L\dot{q}) - \frac{\partial}{\partial q} \left( qV_e - \frac{q^2}{2C} \right) = -\frac{d}{dq} \left( \frac{R\dot{q}^2}{2} \right)$$

$$= \frac{d}{dt} \left[ \frac{\partial}{\partial \dot{q}} \left( \frac{L\dot{q}^2}{2} \right) \right] - \frac{\partial}{\partial q} \left( qV_e - \frac{q^2}{2C} \right) = -\frac{d}{dq} \left( \frac{R\dot{q}^2}{2} \right)$$

Hence we identify  $T \equiv \frac{1}{2} L_e \dot{q}^2$

$$V = -qV_e + \frac{q^2}{2C}, \quad \mathcal{F} = \frac{R\dot{q}^2}{2}$$


Also one co-ordinate  $q_i$  for each loop  $i$ .  
 $n$  loops means there are  $q_i$  charges,  $i=1, n$ .



$$\therefore L \equiv T - V = \frac{L_e \dot{q}^2}{2} - \frac{q^2}{2C} + V_e q$$

Note:  $\rightarrow$  1 circuit loop gives one co-ordinate.  $n$ -loops give  $n$  coordinates.

Consider the following 2-loop circuit.

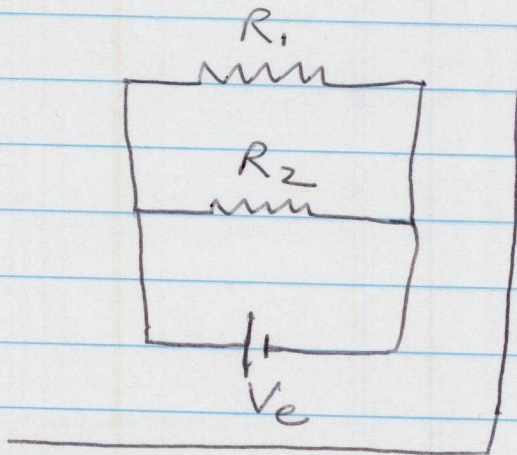

$$\mathcal{F} = \frac{R_1 \dot{q}_1^2}{2} + \frac{R_2 \dot{q}_2^2}{2}$$

$$V = q_1 V_e + q_2 V_e$$

$$\frac{d}{dt} \left( \frac{\partial L}{\partial \dot{q}_i} \right) - \frac{\partial L}{\partial q_i} = -\frac{d\mathcal{F}}{dq_i}$$

where  $i=1, 2$ .

$$\Rightarrow -V_e = -R_1 \dot{q}_1, \quad -V_e = -R_2 \dot{q}_2$$

$$\dot{q}_1 = V_e / R_1, \quad \dot{q}_2 = V_e / R_2$$

$$\text{Total } \dot{q} \equiv \dot{q}_1 + \dot{q}_2 = V_e / R, \quad \text{where } R \equiv \left( \frac{R_1 R_2}{R_1 + R_2} \right)$$

Mechanical Concept

Electrical Concept

Displacement

$\rightarrow$  Charge ( $q$ )

Velocity

$\rightarrow$  Current ( $\dot{q}$ )

Constant Force

$\rightarrow$  ( $V_e$ ) Potential difference

Mass

$\rightarrow$  Inductance ( $L_e$ )

Spring Constant

$\rightarrow$  Reciprocal Capacitance

$k$  in Rayleigh dissipation function  $\mathcal{F}$

$\rightarrow$  ( $1/c$ )

Each Closed loop gives a co-ordinate  $q_i$ .

$\rightarrow$  Resistance ( $R$ )