

DC Circuits

- **Resistance Review**
- **Following the potential around a circuit**
- **Multiloop Circuits**
- **RC Circuits**

Homework for today:

Read Chapters 26, 27

Chapter 26 Questions 1, 3, 10

Chapter 26 Problems 1, 17, 35, 77

Homework for tomorrow:

Chapter 27 Questions 1, 3, 5

Chapter 27 Problems 7, 19, 49


WileyPlus assignment: Chapters 26, 27

Review: Series and Parallel Resistors

Series:

$$R = R_1 + R_2 + R_3$$


Why?

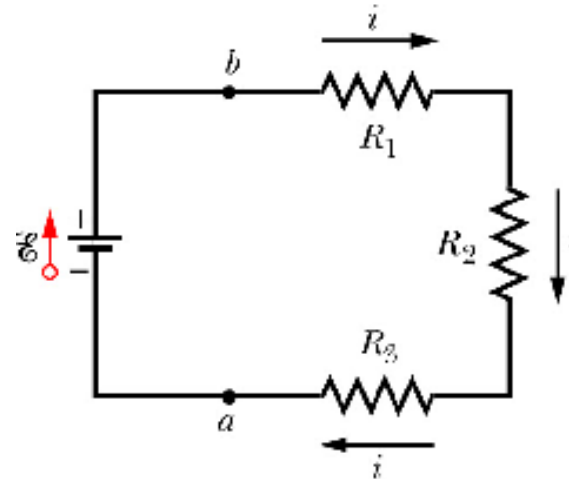

Parallel:



$$1/R = 1/R_1 + 1/R_2 + 1/R_3$$

Why?

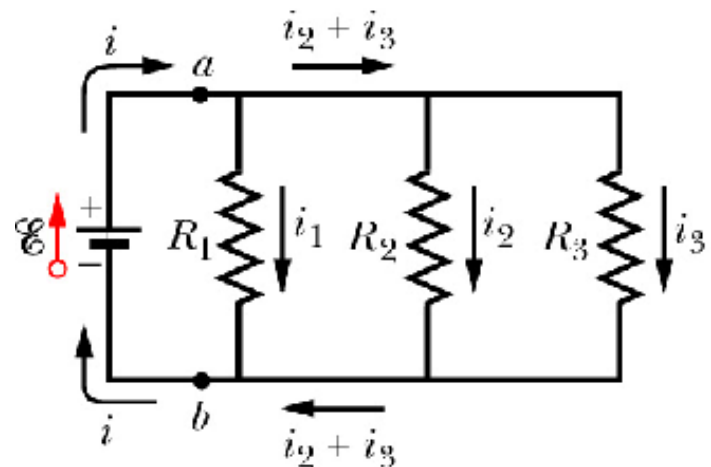


Following the Potential

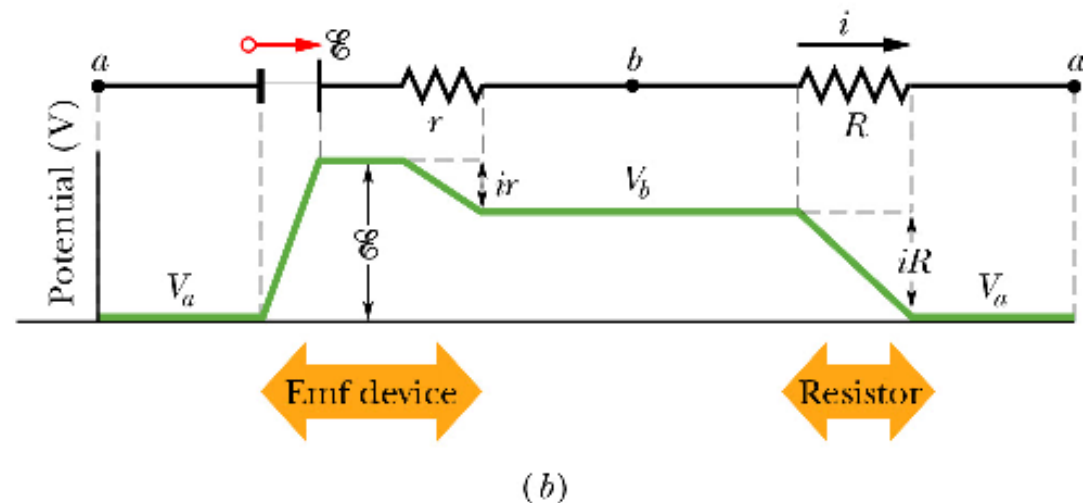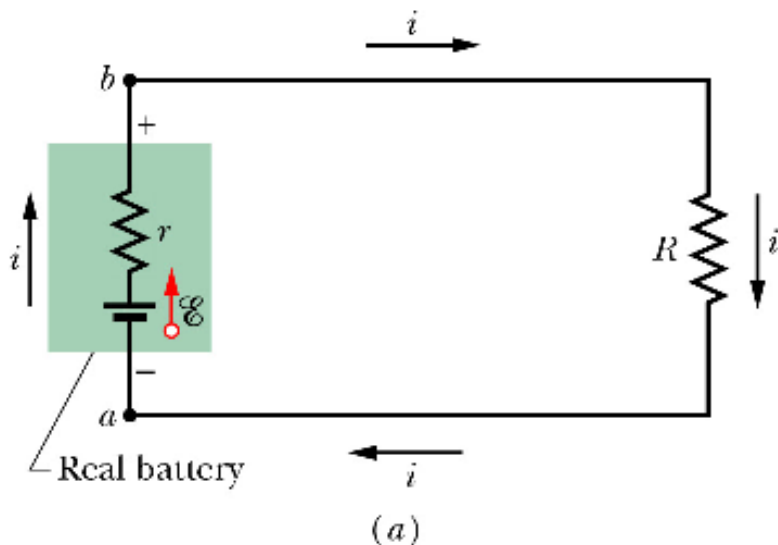Study Fig. 27-4 in the text to see how the potential changes from point to point in a circuit.



Note the net change around the loop is zero.


Following the Potential

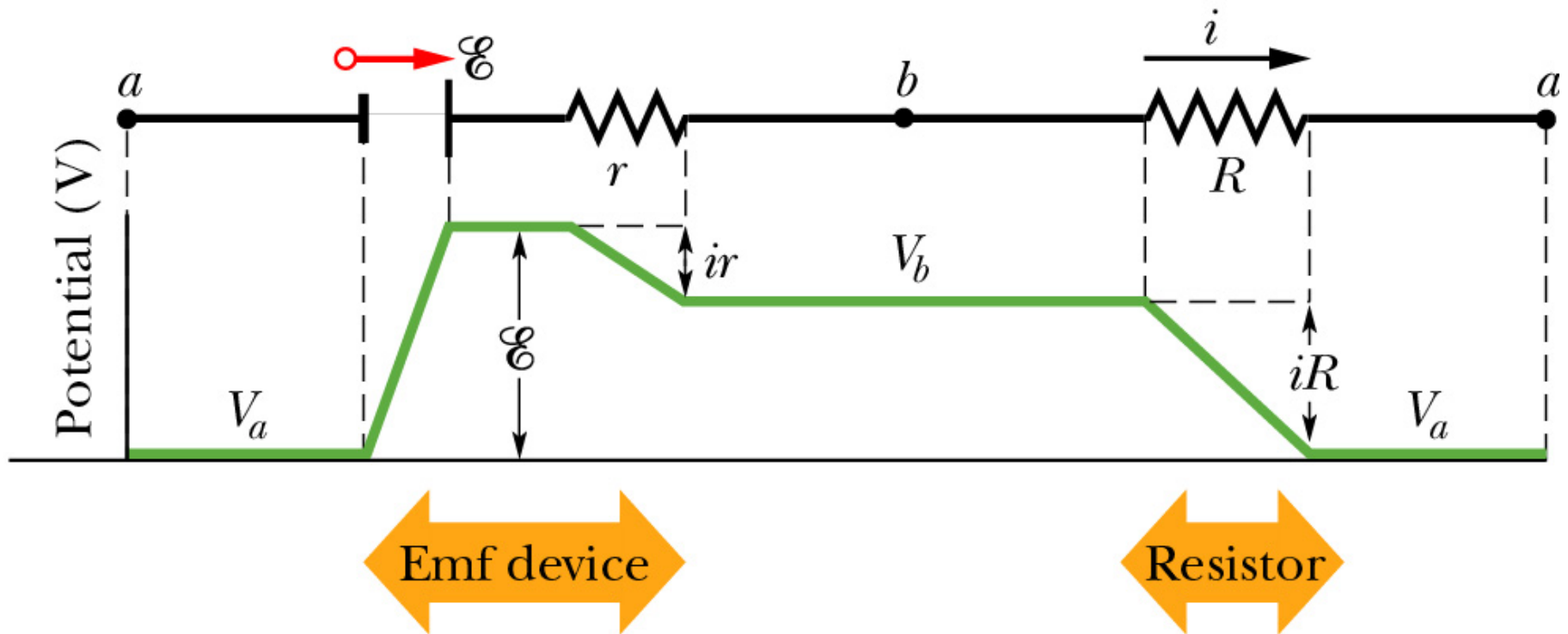

(b)

Note the net change around the loop is zero.


Q.27-1

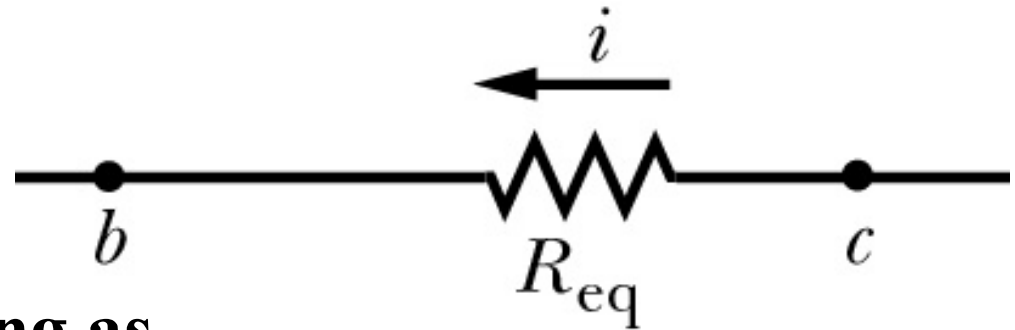

With the current i flowing as shown, which is at the *higher potential*, point b or point c ?

- 1) B is higher
- 2) C is higher
- 3) They are the same
- 4) Not enough information

Solution

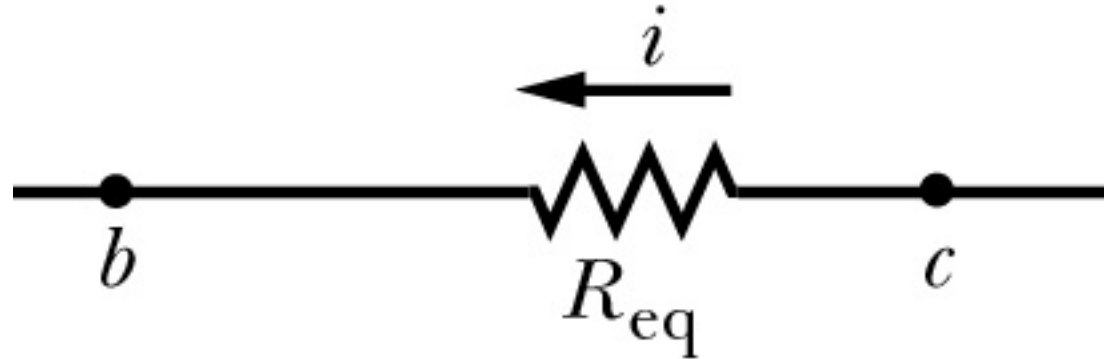

With the current i flowing as shown, which is at the *higher potential*, point b or point c ?

Solution: Current flows from high to low potential just like water flows down hill.


(1) b is higher

(2) c is higher

(3) they're the same

(4) not enough info

Example: Problem 27-30

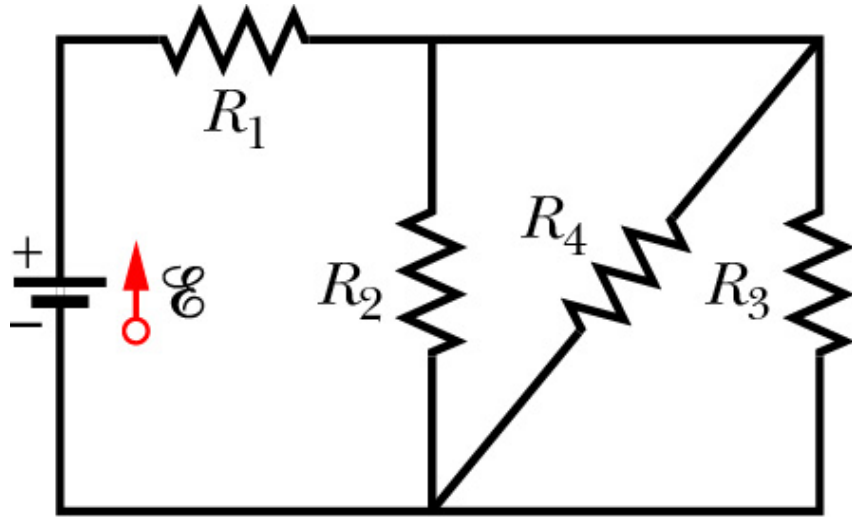


$$\mathcal{E} = 6.0\text{ V} \quad R_1 = 100\ \Omega$$

$$R_2 = R_3 = 50\ \Omega$$

$$R_4 = 75\ \Omega$$

- (a) Find the equivalent resistance of the network.
- (b) Find the current in each resistor.

Problem 27-30 (part a)

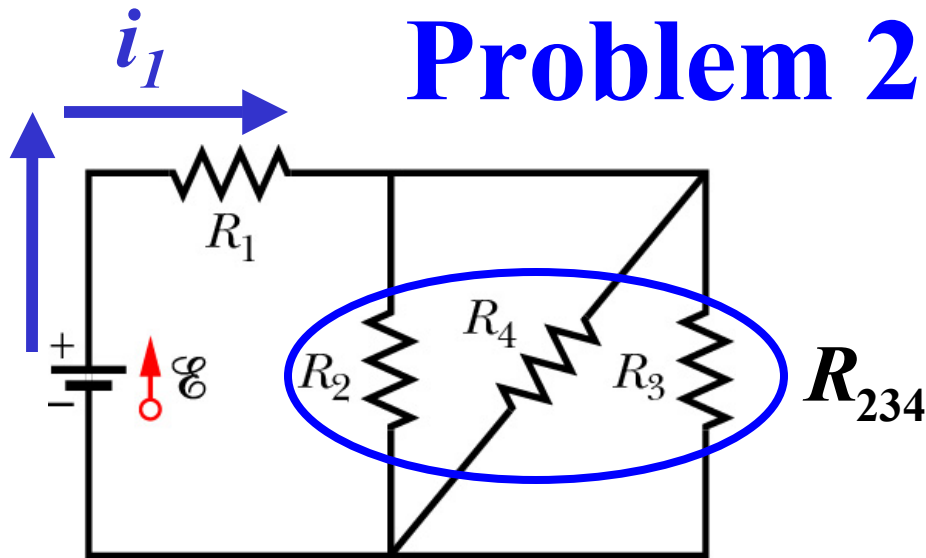

$$\mathcal{E} = 6.0 \text{ V} \quad R_1 = 100 \Omega$$

$$R_2 = R_3 = 50 \Omega$$

$$R_4 = 75 \Omega$$

(a) Find the equivalent resistance of the network.

$$1/R_{234} = 1/R_2 + 1/R_3 + 1/R_4 = 16/300$$

$$\text{So } R_{234} = 300/16 = 19 \Omega$$

Now R_1 and R_{234} are in series so


$$R_{eq} = R_1 + R_{234} = 100 \Omega + 19 \Omega = \underline{119 \Omega}$$

(b) Now current $i_1 = \mathcal{E} / R_{eq} = 50 \text{ mA}$

Problem 27-30 (part b)

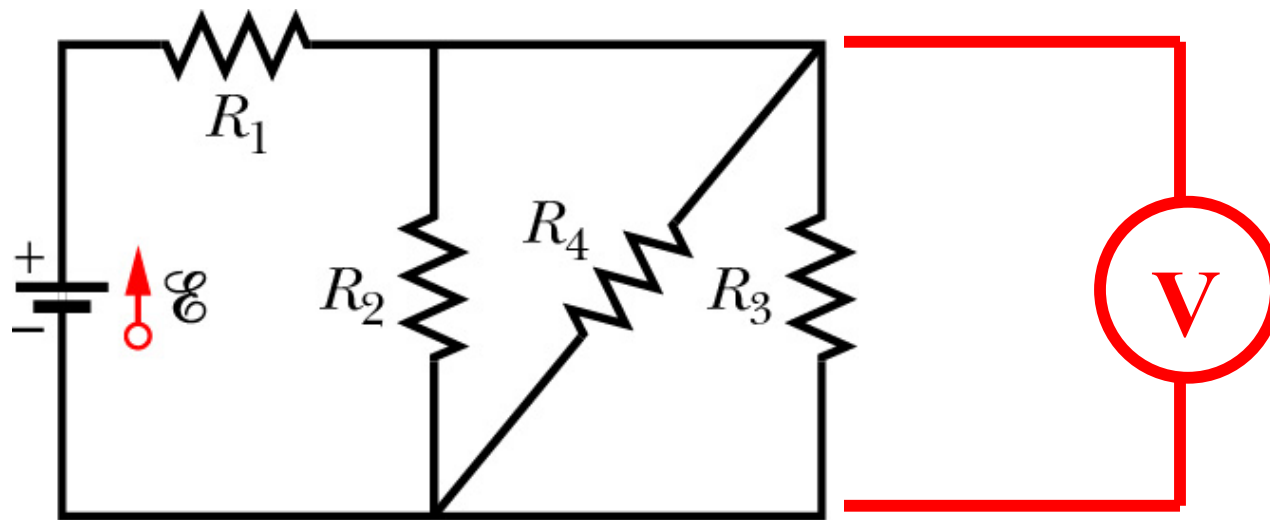(b) Find the current in each resistor.

First note that $i_2 R_2 = i_3 R_3 = i_4 R_4$.



$$\begin{aligned} V &= i R_{234} \\ &= .050 \text{ A} \times 19 \Omega \\ &= 0.95 \text{ V} \end{aligned}$$

So

$$\begin{aligned} i_2 &= V / R_2 = .95 / 50 = 19 \text{ mA} \\ i_3 &= V / R_3 = .95 / 50 = 19 \text{ mA} \\ i_4 &= V / R_4 = .95 / 75 = 12 \text{ mA} \end{aligned}$$

Check: These three add up to $i_1 = 50 \text{ mA}$.


Q.27-2

$$R_2 = 2\ \Omega$$

$$R_3 = 3\ \Omega$$


$$i_2 = 6\ A$$

$$i_3 = ?$$

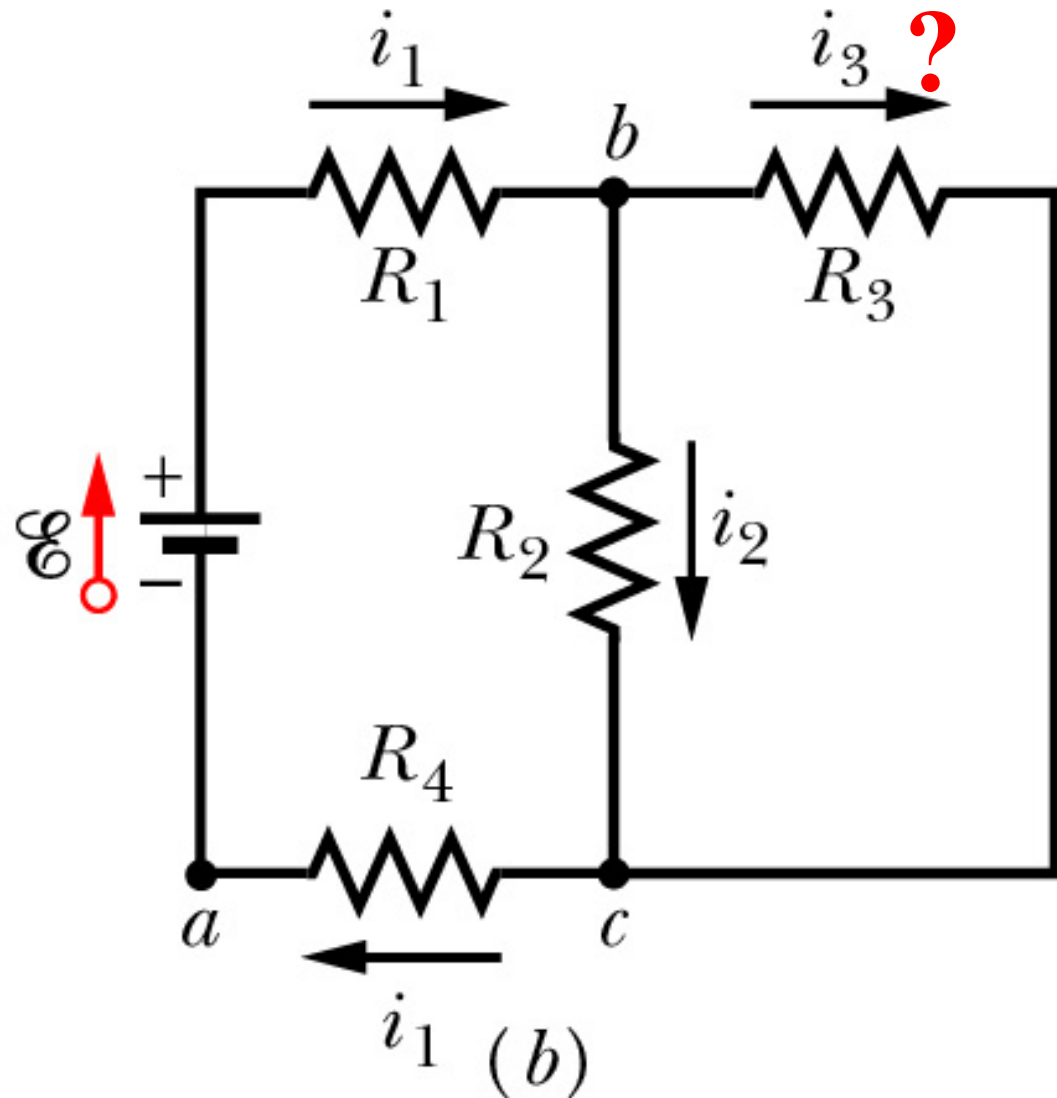

Calculate i_3 , find the closest single-digit number (0-9).

Q.27-2

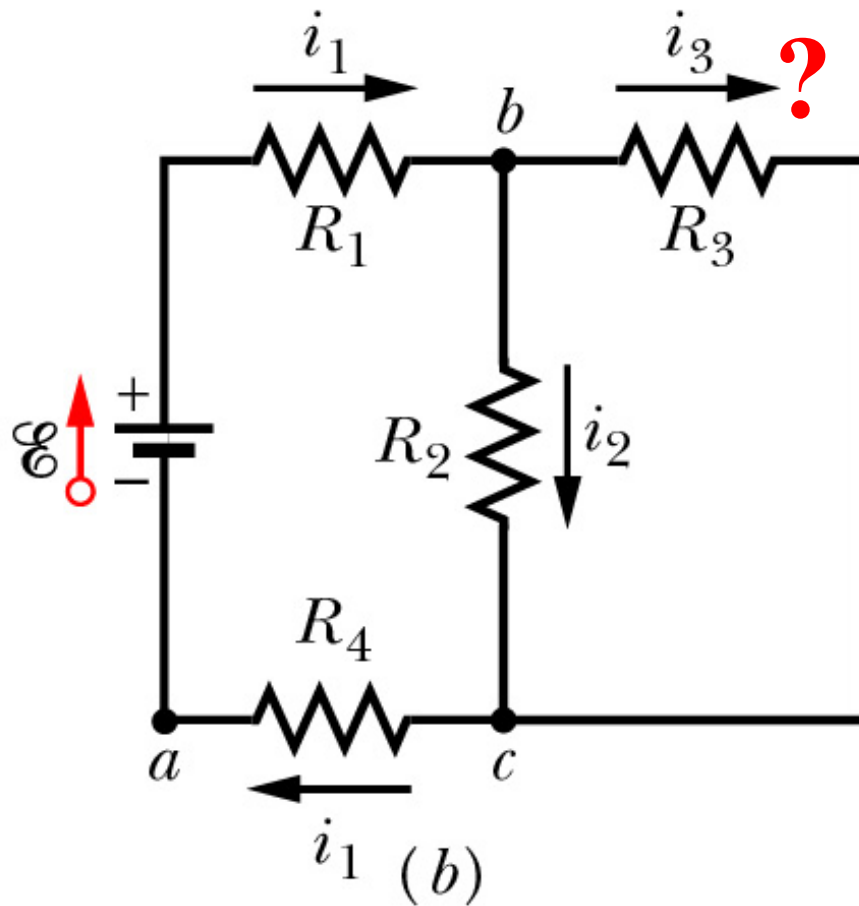

$$R_2 = 2 \Omega$$

$$R_3 = 3 \Omega$$

$$i_2 = 6 \text{ A}$$

$$i_3 = ?$$


- 1) 1 A
- 2) 2 A
- 3) 3 A
- 4) 4 A
- 5) 5 A
- 6) 6 A
- 7) 7 A
- 8) 8 A
- 9) 9 A

Q.27-2

$$R_2 = 2\ \Omega$$

$$R_3 = 3\ \Omega$$

$$i_2 = 6\ A$$

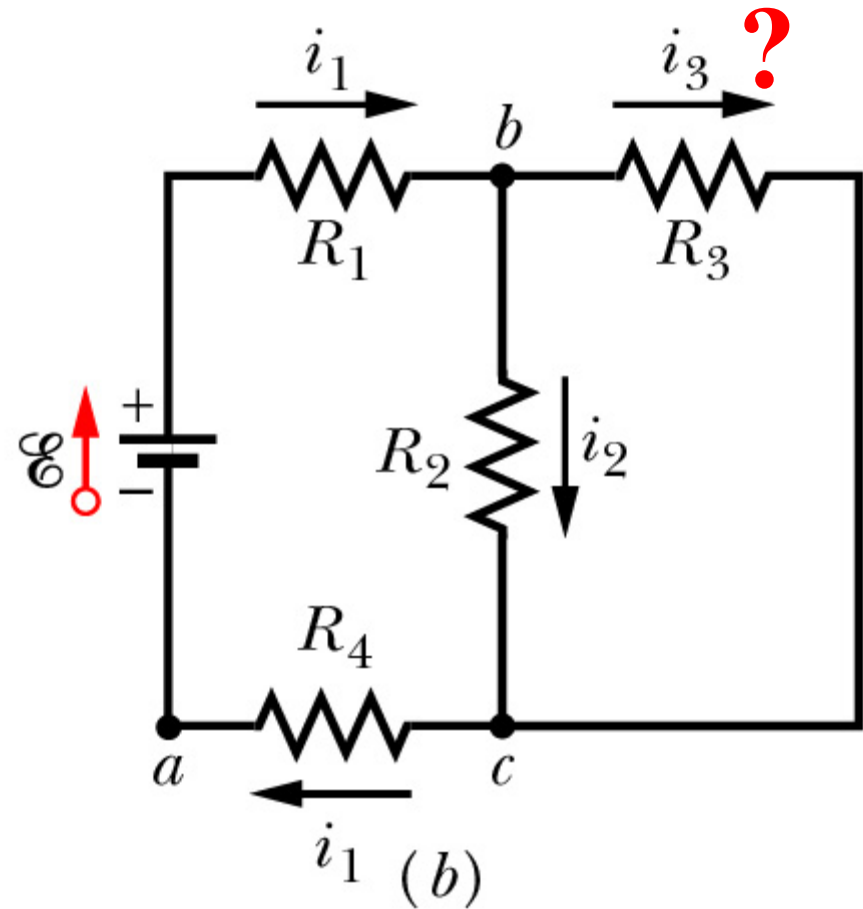

$$V_b - V_c = i_2 R_2 = i_3 R_3$$

$$\therefore i_3 = \frac{i_2 R_2}{R_3} = \frac{2}{3} i_2 = 4\ A$$

4

More Complicated Circuits

How do we solve a problem with more than one emf and several loops? We can't do it just by series and parallel resistor combinations.




Rules for Multiloop Circuits

- *The net voltage change around any loop is zero.*
“Energy conservation”
- *The net current into any junction is zero.*
“Charge conservation”

Using these two rules we can always get enough equations to solve for the currents if we are given the emfs and resistances.

Example

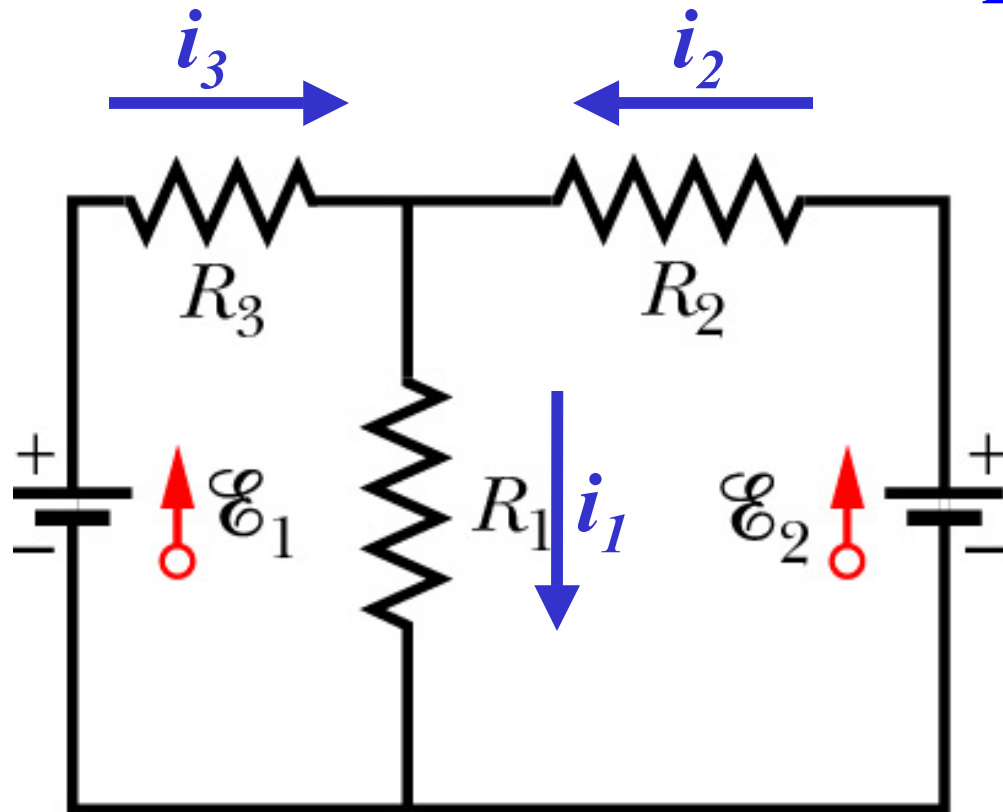

$$\mathcal{E}_1 = 24V$$

$$\mathcal{E}_2 = 12V$$


$$R_1 = 5\Omega$$

$$R_2 = R_3 = 30\Omega$$

Find all currents!

First define unknowns: i_1, i_2, i_3

Example (continued)

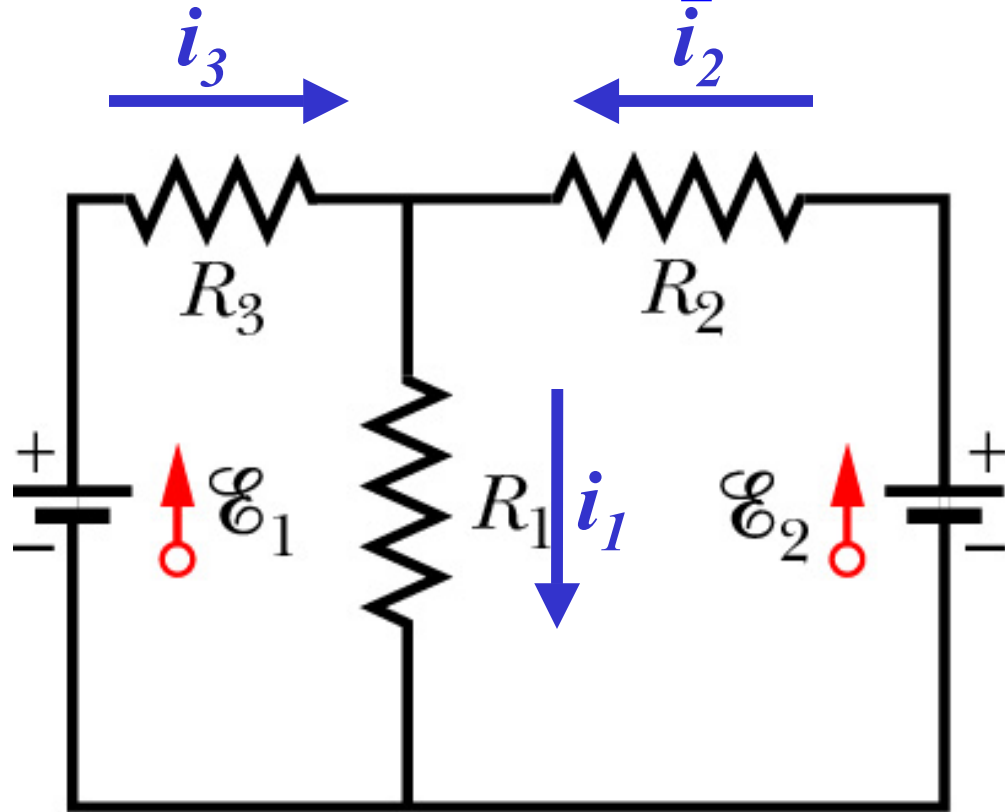

Left-hand loop:

$$\mathcal{E}_1 - i_3 R_3 - i_1 R_1 = 0$$

Right-hand loop:

$$\mathcal{E}_2 - i_2 R_2 - i_1 R_1 = 0$$

Junction:

$$i_1 = i_2 + i_3$$

Algebra: solve 3 equations for 3 unknowns i_1, i_2, i_3

Loop and junction equations:

$$\mathcal{E}_1 - i_3 R_3 - i_1 R_1 = 0 \qquad i_1 = i_2 + i_3$$

$$\mathcal{E}_2 - i_2 R_2 - i_1 R_1 = 0$$

Put in the given numbers and also replace i_1 by $i_2 + i_3$:

$$5i_1 + 30i_3 = 5i_2 + 35i_3 = 24$$


$$5i_1 + 30i_2 = 35i_2 + 5i_3 = 12$$

Solve two equations in two unknowns to get:

$$i_2 = 250 \text{ mA} \qquad i_3 = 650 \text{ mA}$$

Add to get
$$i_1 = i_2 + i_3 = 900 \text{ mA}$$


Check by using outer loop:

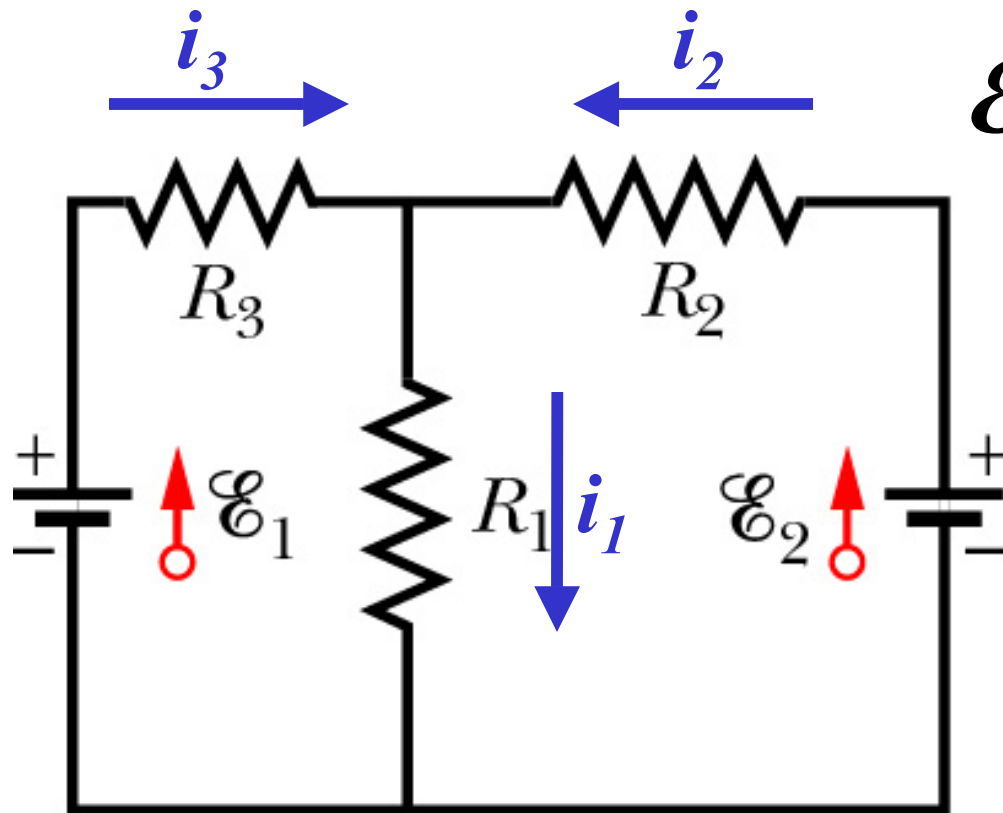

$$\mathcal{E}_1 - i_3 R_3 + i_2 R_2 - \mathcal{E}_2 = 0 ?$$

$$\begin{aligned} 24 - 30(.65 - .25) - 12 \\ &= 12 - 30 \times .40 \\ &= 12 - 12 \\ &= 0 \end{aligned}$$

Repeat with a different R_1

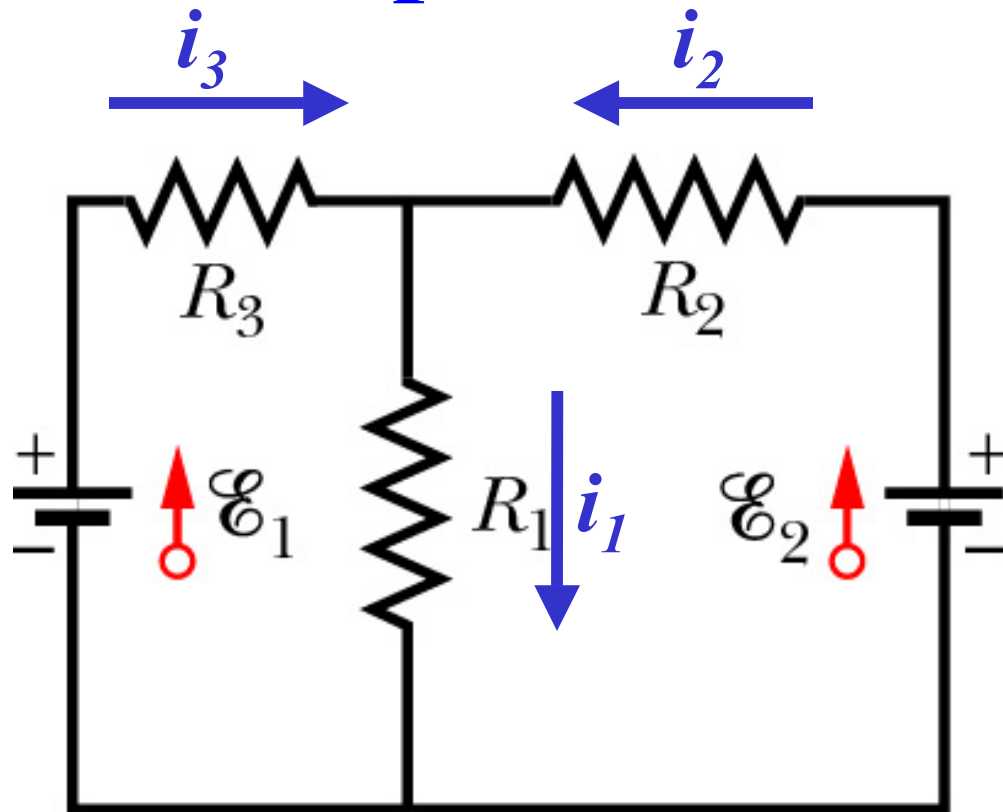

$$\mathcal{E}_1 = 24V$$

$$\mathcal{E}_2 = 12V$$

$$R_1 = 40\Omega$$

$$R_2 = R_3 = 30\Omega$$



Exercise for the student: Same equations give negative i_2 in this case! This means current going downward through right-hand battery.

Back to Basics

- **Examples that don't involve so much algebra, but focus on the ideas of current and voltage.**
- **Even though you have a multiloop circuit so you need to write down the equations from the loop rule and the junction rule, you may not have to actually solve simultaneous equations.**




Simpler Examples

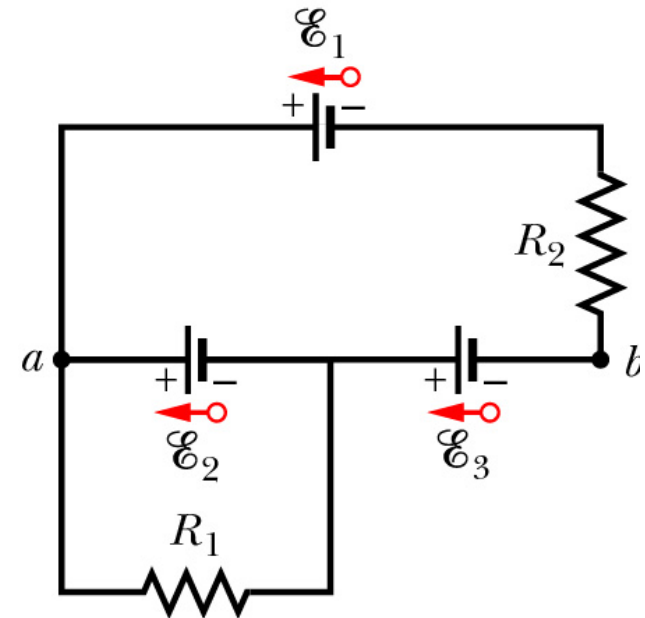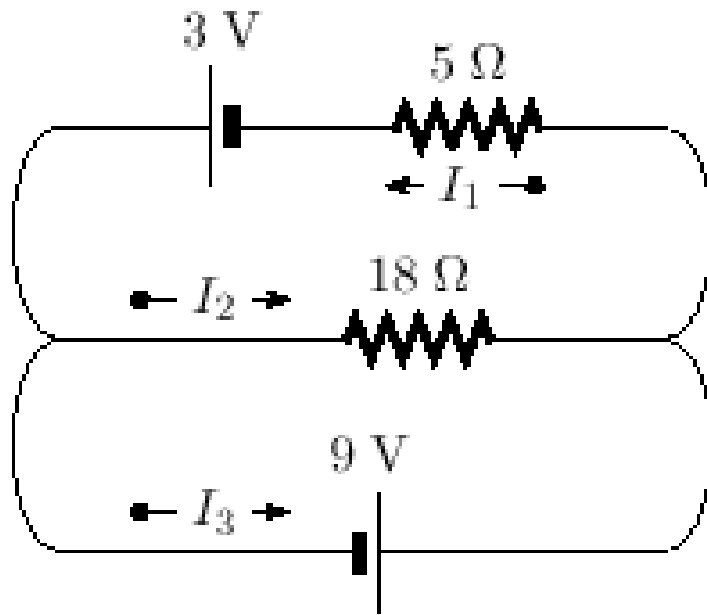

Textbook homework
problem 27-19

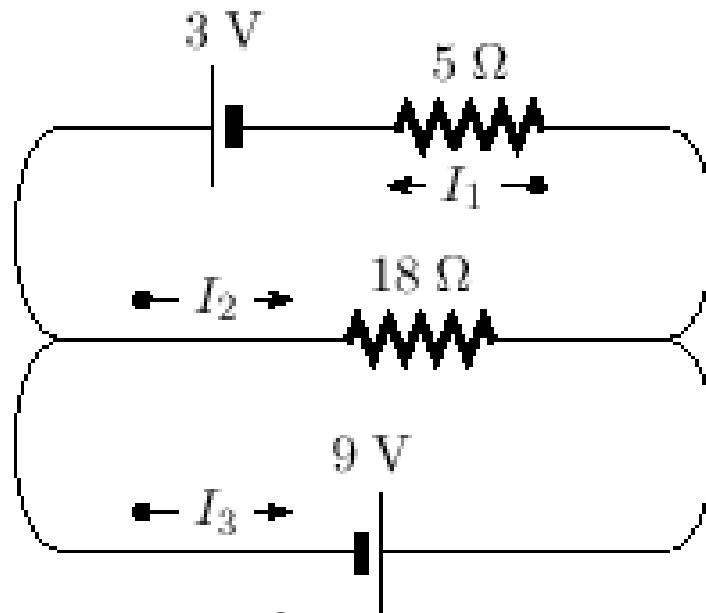Both these problems can be solved for *one unknown at a time*, without messy algebra.



$$9 + 18 \times I_2 = 0 \quad I_2 = -0.5 \text{ A}$$


$$9 - 5 \times I_1 + 3 = 0 \quad I_1 = \frac{12}{5} = 2.4 \text{ A}$$

$$I_3 = I_1 - I_2 = 2.9 \text{ A}$$

Check:

$$P_{in} = 9I_3 + 3I_1 = 33.3 \text{ W} \quad P_{out} = 5I_1^2 + 18I_2^2 = 33.3 \text{ W}$$

Discharging a Capacitor

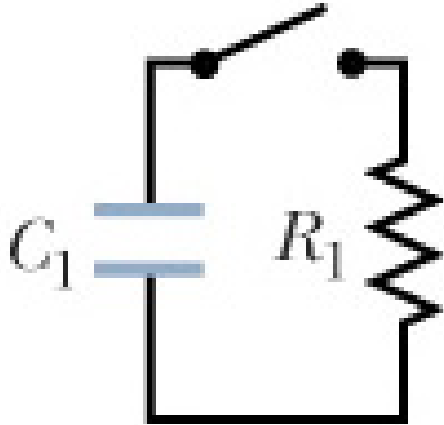

Capacitor has charge Q_0 .

At time $t=0$, close switch.

What is charge $q(t)$ for $t>0$?

Obviously $q(t)$ is a function which decreases gradually, approaching zero as t approaches infinity.



What function would do this?

$$q(t) = Q_0 e^{-t/\tau}$$

But what is the time constant ♦?

Analyze circuit equation: find $\tau = RC$

Charging a Capacitor

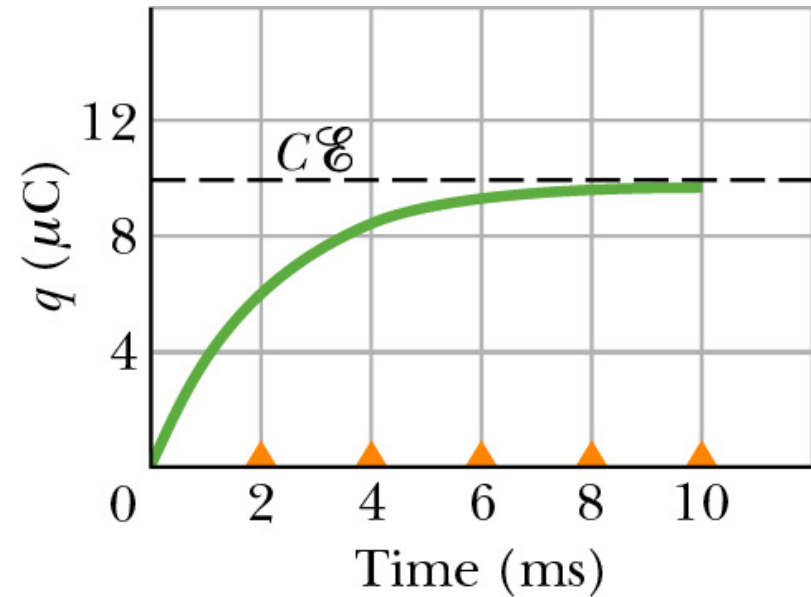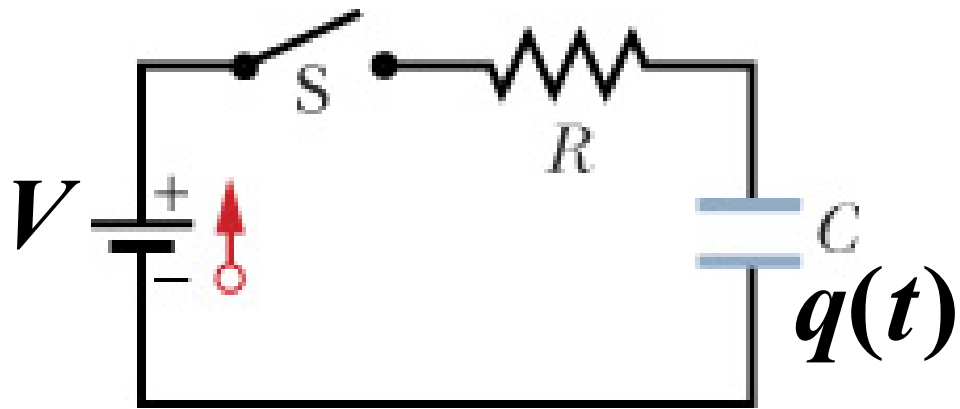


(a)

For small t , $q=0$ and $i=V/R$.

For large t , $q=CV$ and $i=0$.

$$q(t) = CV \left[1 - e^{-t/\tau} \right]$$

$$\tau = RC$$

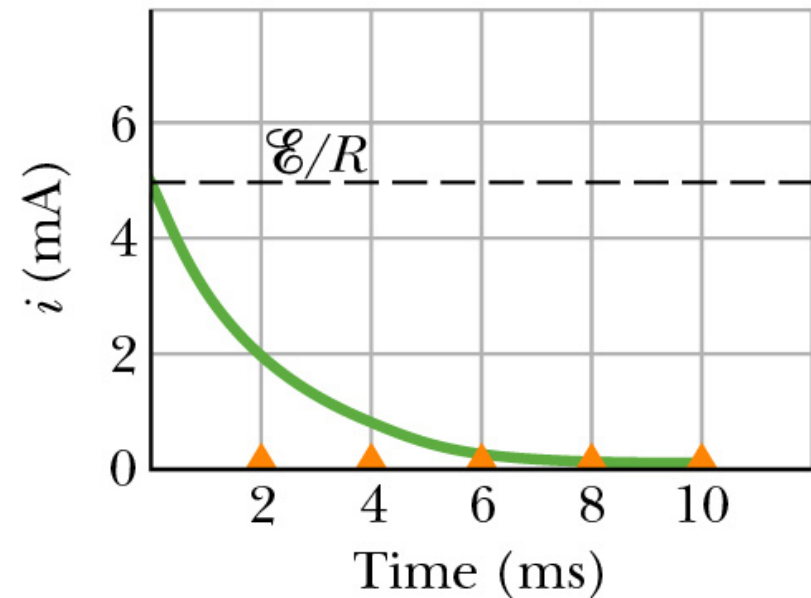

(b)

DC Circuits II

- **Circuits Review**
- **RC Circuits**
- **Exponential growth and decay**

Circuits review so far


- **Resistance and resistivity** $R = \rho l / A$
- **Ohm's Law and voltage drops** $\Delta V = -iR$
- **Power and Joule heating** $P = iV$
- **Resistors in series and parallel**
- **Loop and junction rules**

Review: Series and Parallel Resistors

Series:

$$R = R_1 + R_2 + R_3$$


Why?

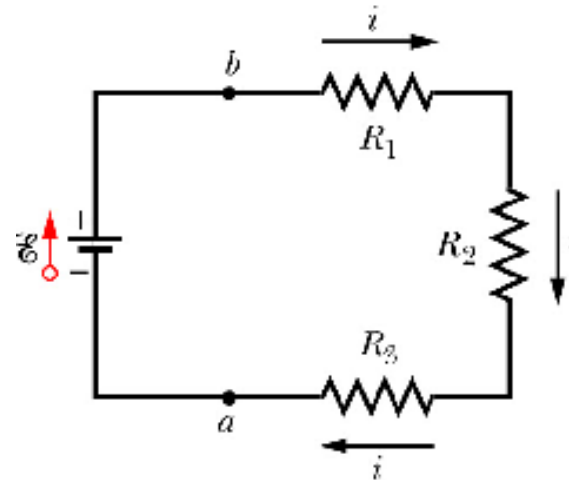

Parallel:

$$1/R = 1/R_1 + 1/R_2 + 1/R_3$$

Why?

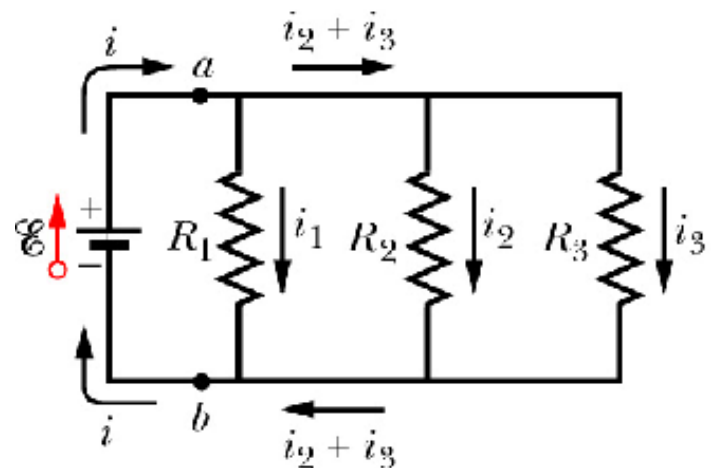


Review: Rules for Multiloop Circuits

- *The net voltage change around any loop is zero.*
“Energy conservation”
- *The net current into any junction is zero.*
“Charge conservation”

Using these two rules we can always get enough equations to solve for the currents if we are given the emfs and resistances.

Review example

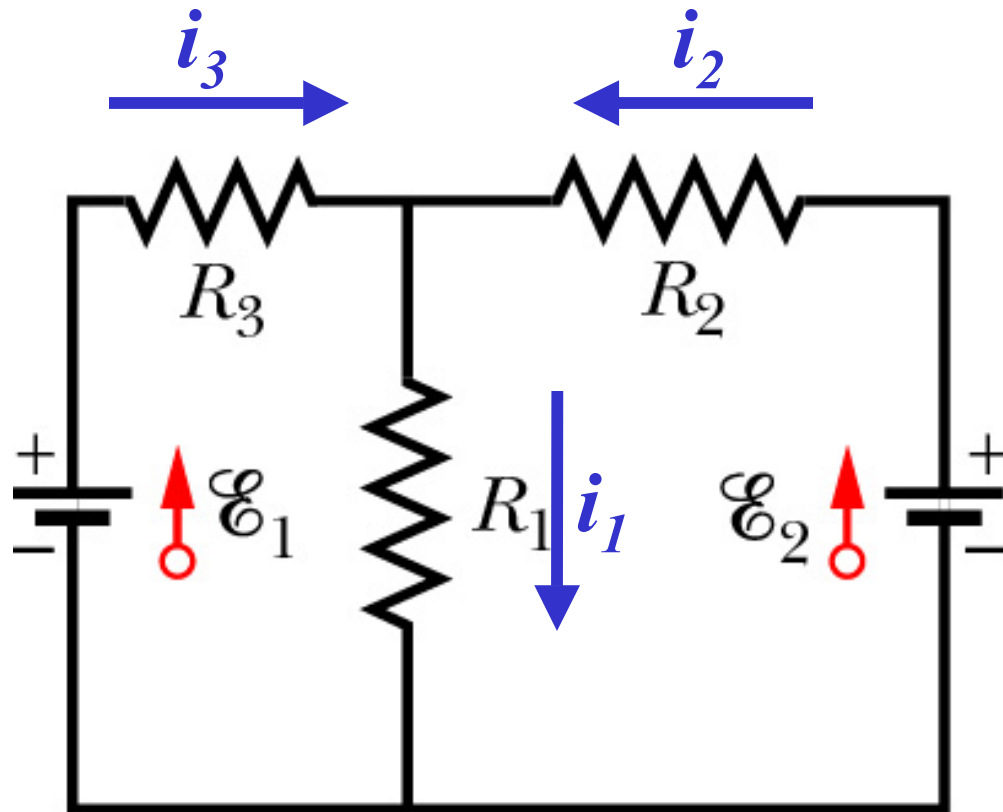

Left-hand loop:

$$\mathcal{E}_1 - i_3 R_3 - i_1 R_1 = 0$$

Right-hand loop:

$$\mathcal{E}_2 - i_2 R_2 - i_1 R_1 = 0$$



Junction:

$$i_1 = i_2 + i_3$$

Algebra: solve 3 equations for 3 unknowns i_1, i_2, i_3

If any $i < 0$, current flows the opposite direction.

Simpler Examples

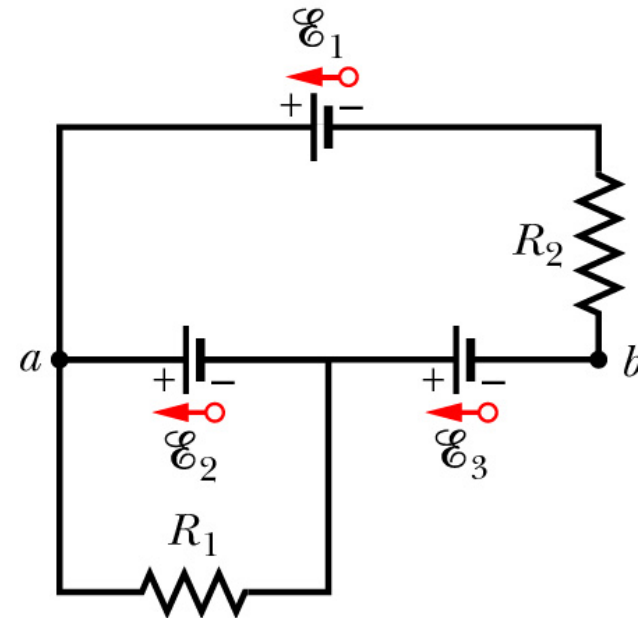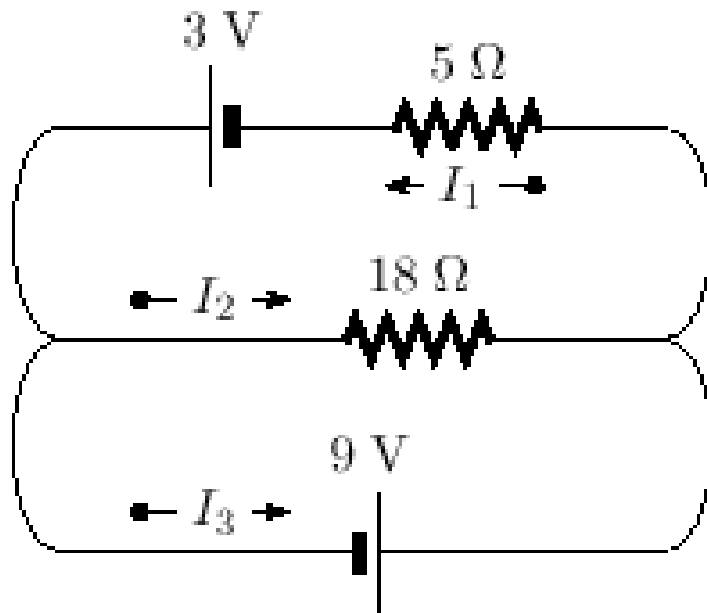

Textbook homework
problem 27-19

Both these problems can be solved for *one unknown at a time*, without messy algebra.

Q.27-3

Resistors R_1 and R_2 are connected in series.
If $R_2 > R_1$, what can you say about the
resistance R of the combination?

1. $R > R_2$
2. $R_2 > R > R_1$
3. $R_1 > R$
4. None of the above

Q.27-3

- Resistors R_1 and R_2 are connected in series.
- $R_2 > R_1$.
- What can you say about the resistance R of this combination?

Solution:

$$R = R_1 + R_2 \quad \text{so} \quad R > R_2$$

$$(1) R > R_2$$

$$(2) R_2 > R > R_1$$

$$(3) R_1 > R$$

(4) *None of the above*

Q.27-4

Resistors R_1 and R_2 are connected in parallel.
If $R_2 > R_1$, what can you say about the
resistance R of the combination?

1. $R > R_2$
2. $R_2 > R > R_1$
3. $R_1 > R$
4. None of the above

Q.27-4

- Resistors R_1 and R_2 are connected in parallel.
- $R_2 > R_1$.
- What can you say about the resistance R of this combination?

Solution:
$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} \quad \text{so} \quad \frac{1}{R} > \frac{1}{R_1}$$


(1) $R > R_2$

(2) $R_2 > R > R_1$

(3) $R_1 > R$

(4) *None of the above*

Discharging a Capacitor

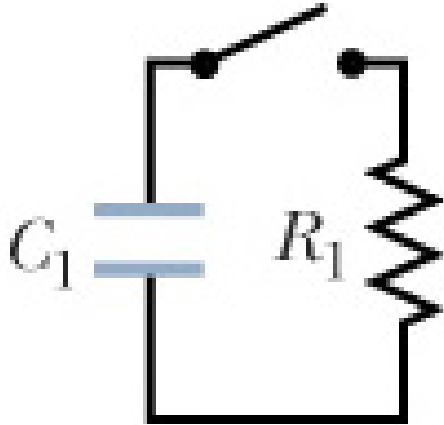

Capacitor has charge Q_0 .

At time $t=0$, close switch.

What is charge $q(t)$ for $t>0$?

Obviously $q(t)$ is a function which decreases gradually, approaching zero as t approaches infinity.


What function would do this?

$$q(t) = Q_0 e^{-t/\tau}$$

But what is the time constant ♦?

Analyze circuit equation: find $\tau = RC$

Discharging a Capacitor

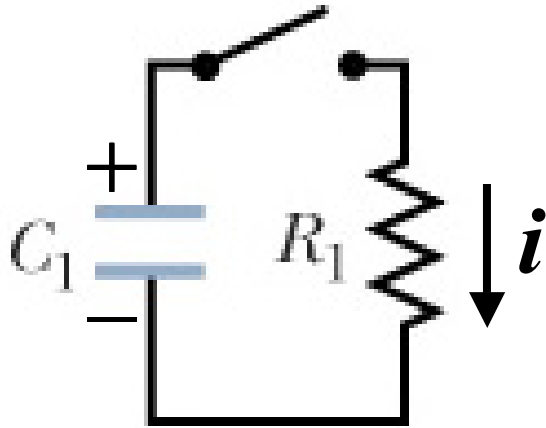

Sum voltage changes around loop:

$$Q/C - iR = 0, \quad i = \frac{Q}{RC}$$

But

$$i = -\frac{dQ}{dt}$$

Get *differential equation* for $Q(t)$:


$$\frac{dQ}{dt} = -\frac{Q}{RC}$$

Solution:

$$Q(t) = Q_0 e^{-t/\tau}$$

Where τ is the time constant $\tau = RC$


Charging a Capacitor

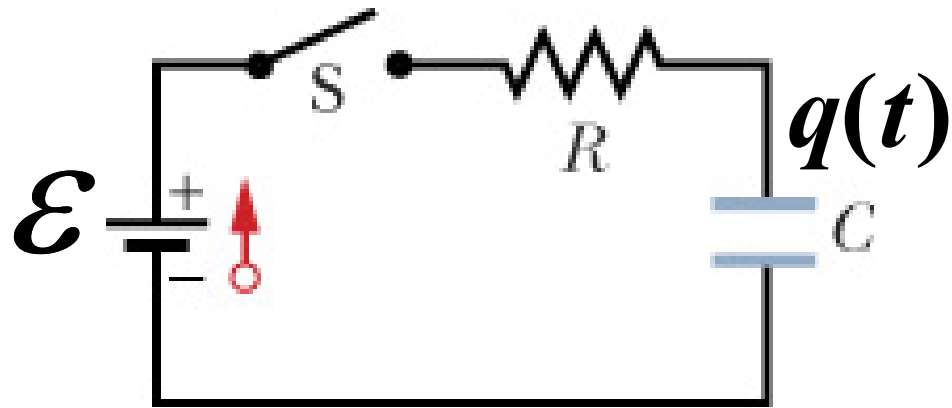


For small t , $q=0$ and $i = \mathcal{E} / R$

For large t , $i=0$ and $q = C\mathcal{E}$

But what are $q(t)$, $i(t)$?

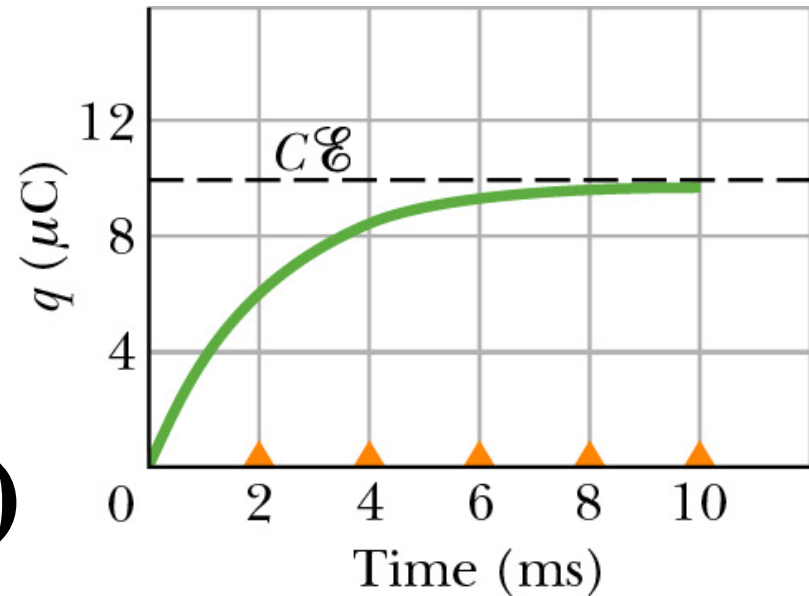

(a)

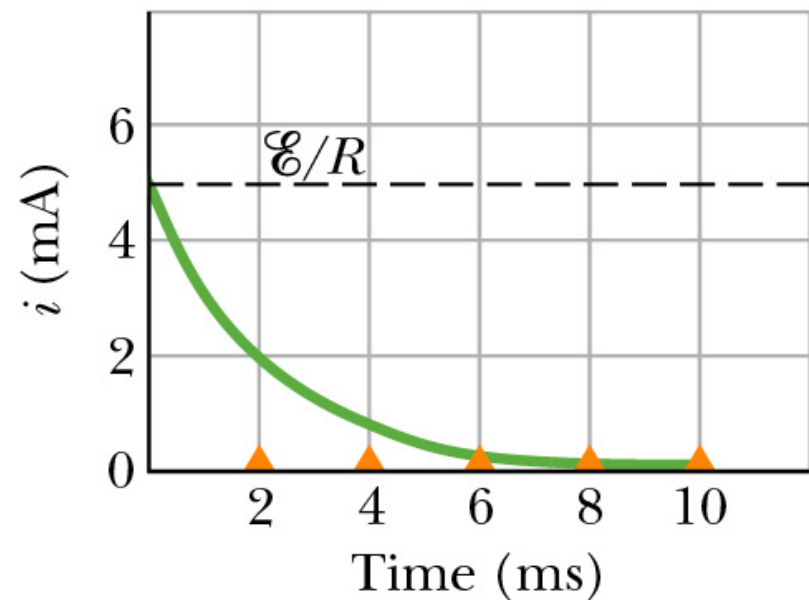

(b)

Charging a Capacitor

Sum voltage changes:

$$\mathcal{E} - iR - Q/C = 0$$

$$i = \frac{dQ}{dt}$$


Get diff. eq.:

$$\frac{dQ}{dt} = \frac{\mathcal{E}}{R} - \frac{Q}{RC}$$

Solution

$$Q(t) = C\mathcal{E} \left(1 - e^{-t/\tau} \right)$$

$$\tau = RC$$

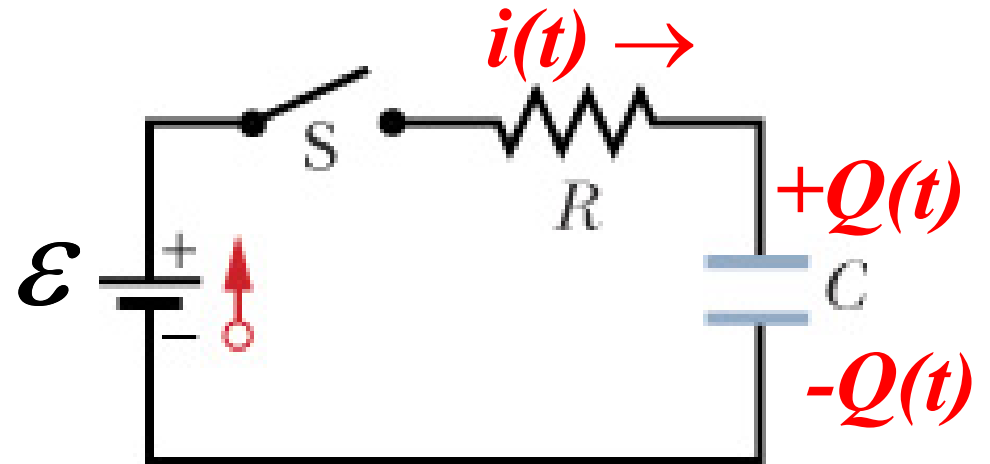


Charging a Capacitor

See solution gives desired behavior:


$$Q(t) = C\mathcal{E} \left(1 - e^{-t/\tau} \right)$$

$\rightarrow 0$ as $t \rightarrow 0$

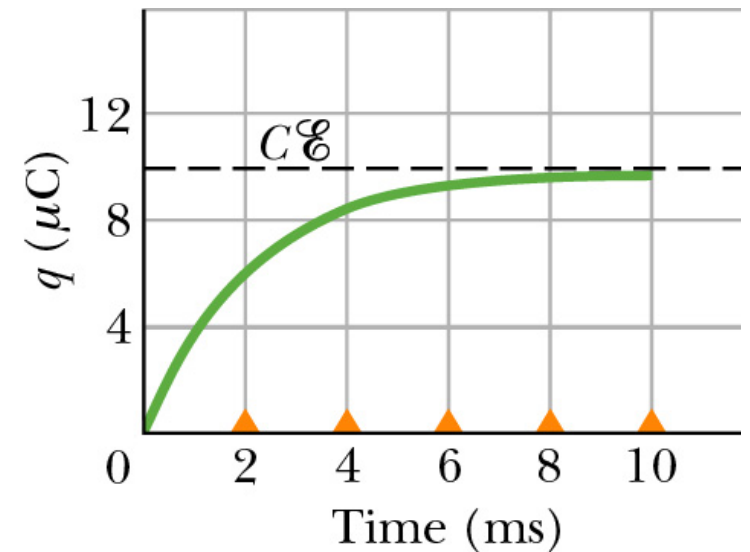$\rightarrow C\mathcal{E}$ as $t \rightarrow \infty$



(a)

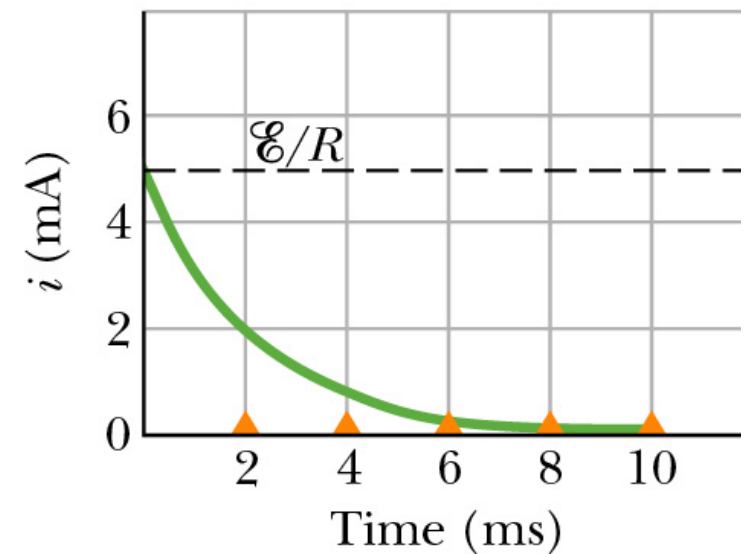

(b)

Exponential Growth and Decay

This *simple differential equation* occurs in many situations:

$$\frac{dQ}{dt} = (\text{Const.}) Q$$

If $dQ/dt = +KQ$, we have the “snowball” equation: growth rate proportional to size. *Population growth.*


$$\frac{dQ}{dt} = +KQ \quad \longrightarrow \quad Q = Q_0 e^{+Kt}$$

If $dQ/dt = -KQ$, we have rate of *decrease* proportional to size. For example *radioactive decay.*

$$\frac{dQ}{dt} = -KQ \quad \longrightarrow \quad Q = Q_0 e^{-Kt}$$

Try Exponential Solution

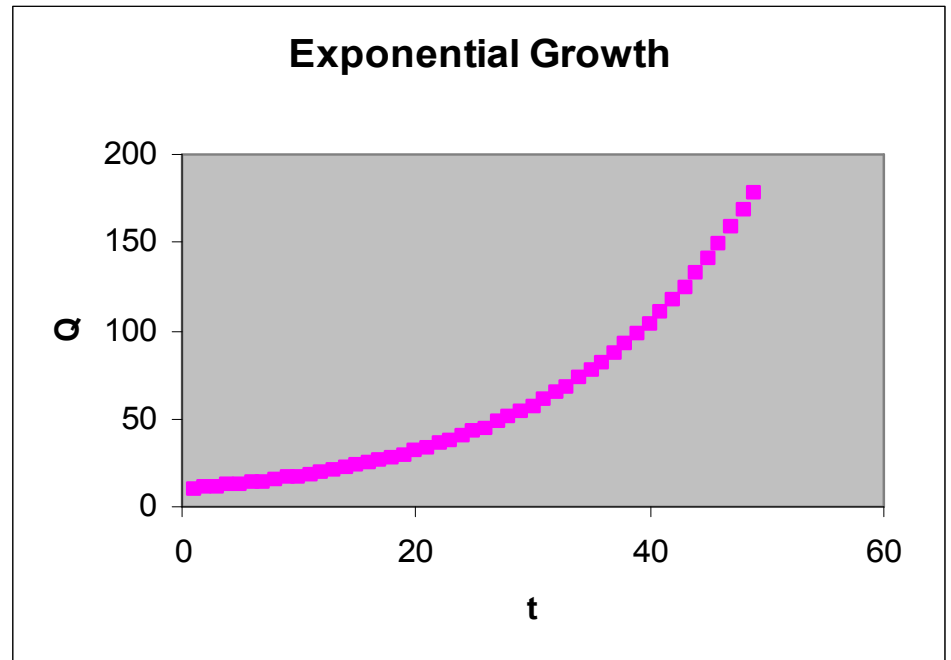We know we want a result which increases faster and faster. One function which does this is the exponential function. So try that:



To solve $\frac{dQ}{dt} = KQ$ *try* $Q(t) = Q_0 e^{t/\tau}$

Questions:

1. Is this a solution?
2. If so, what is the “*time constant*” τ ?

To solve $\frac{dQ}{dt} = KQ$ try $Q(t) = Q_0 e^{t/\tau}$

$$Q(t) = Q_0 e^{t/\tau}$$

$$\frac{dQ}{dt} = Q_0 \frac{d}{dt} e^{t/\tau} = \frac{Q_0}{\tau} e^{t/\tau} = \frac{Q}{\tau}$$

But we want $\frac{dQ}{dt} = KQ$

So we **DO** have a solution **IF**

$$\tau = 1 / K$$

Doubling Time

If $Q(t) = Q_0 e^{t/\tau}$

how long does it take for Q to double?

$$\frac{Q(t + \Delta t)}{Q(t)} = \frac{e^{(t+\Delta t)/\tau}}{e^{t/\tau}} = e^{\Delta t/\tau}$$

And $e^{\Delta t/\tau} = 2$ *if* $\Delta t / \tau = \ln(2) = 0.693$

So $\Delta t \cong 0.7 \tau$

Radioactive Decay

For an unstable isotope, a certain fraction of the atoms will disintegrate per unit time.

$$\text{For } \frac{dQ}{dt} = -KQ \quad \text{use } Q(t) = Q_0 e^{-t/\tau}$$

Now τ is called the mean life, and the half-life is $T_{1/2} = \tau \ln(2) =$ time for half the remaining atoms to disintegrate, and

$$T_{1/2} \cong 0.7 \tau$$

Discharge of a Capacitor

Back to electricity. From the loop rule we got

$$\frac{dQ}{dt} = -\frac{Q}{RC} = -KQ$$

So the solution is $Q(t) = Q_0 e^{-t/\tau}$

But what are Q_0 and τ ?

Initial condition: $Q_0 = Q(0)$

Time constant: $\tau = 1/K =$ RC

Example

A 40 pF capacitor with a charge of 20 nC is discharged through a 50 MΩ resistor.

(a) What is the time constant?

$$\tau = RC = 40 \times 10^{-12} \times 50 \times 10^6 = 2.0 \times 10^{-3} \text{ s}$$

(b) At what time will ½ the charge remain?

$$T_{1/2} = 0.7\tau = 0.7 \times 2.0 \times 10^{-3} \text{ s} = 1.4 \text{ ms}$$

(c) How much charge will remain after 5 ms?

$$Q(t) = Q_0 e^{-t/\tau} = 20 \times e^{-2.5} = 1.64 \text{ nC}$$

Circuits Summary

Things to remember about DC circuits:

- Resistance and resistivity $R = \rho l / A$
- Ohm's Law and voltage drops $\Delta V = -iR$
- Power and Joule heating $P = iV$
- Resistors in series and parallel
- Loop and junction rules
- RC circuits: charging and discharging a capacitor
- RC time constant $Q(t) = Q_0 e^{-t/\tau} \quad \tau = RC$

Quiz tomorrow on Chapters 26,27.