

DC Circuits

M 2/6/06

- Resistance Review
- Following the potential around a circuit
- Multiloop Circuits
- RC Circuits

Homework for today:

Read Chapters 26, 27

Chapter 26 Questions 1, 3, 10

Chapter 26 Problems 1, 17, 18, 35, 77

Homework for tomorrow:

Chapter 27 Questions 1, 3, 5


Chapter 27 Problems 7, 19, 49

WileyPlus assignment: Chapters 26, 27

Review: Series and Parallel Resistors

Series:


$$R = R_1 + R_2 + R_3$$

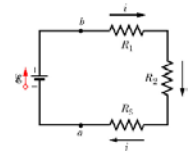

Why?

Parallel:


$$1/R = 1/R_1 + 1/R_2 + 1/R_3$$

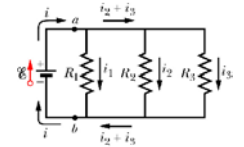

Why?


Following the Potential

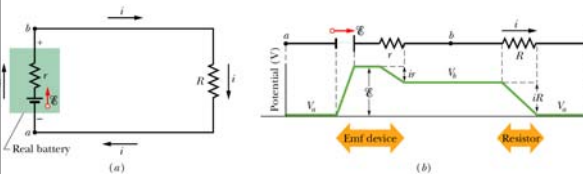Study Fig. 27-4 in the text to see how the potential changes from point to point in a circuit.




Note the net change around the loop is zero.

Following the Potential

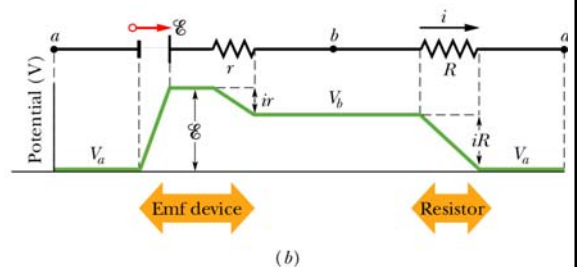

Note the net change around the loop is zero.


Q.27-1

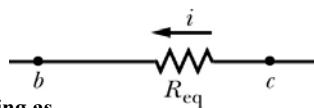

With the current i flowing as shown, which is at the *higher potential*, point b or point c ?

- 1) B is higher
- 2) C is higher
- 3) They are the same
- 4) Not enough information

Solution

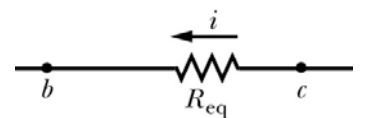


With the current i flowing as shown, which is at the *higher potential*, point b or point c ?

Solution: Current flows from high to low potential just like water flows down hill.

- (1) b is higher
- (2) c is higher
- (3) they're the same
- (4) not enough info


Example: Problem 27-30

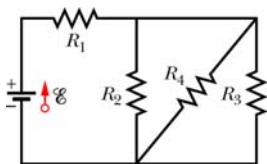

$$\begin{aligned} \mathcal{E} &= 6.0V & R_1 &= 100\Omega \\ R_2 &= R_3 & &= 50\Omega \\ R_4 &= 75\Omega & & \end{aligned}$$

- (a) Find the equivalent resistance of the network.
 (b) Find the current in each resistor.

Problem 27-30 (part a)

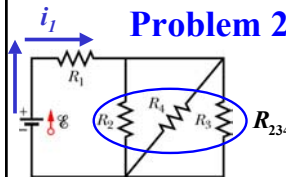

$$\begin{aligned} \mathcal{E} &= 6.0V & R_1 &= 100\Omega \\ R_2 &= R_3 & &= 50\Omega \\ R_4 &= 75\Omega & & \end{aligned}$$

- (a) Find the equivalent resistance of the network.

$$1/R_{234} = 1/R_2 + 1/R_3 + 1/R_4 = 16/300$$

$$\text{So } R_{234} = 300/16 = 19\Omega$$

Now R_1 and R_{234} are in series so


$$R_{eq} = R_1 + R_{234} = 100\Omega + 19\Omega = \underline{119\Omega}$$

- (b) Now current $i_1 = \mathcal{E} / R_{eq} = 50 \text{ mA}$

Problem 27-30 (part b)

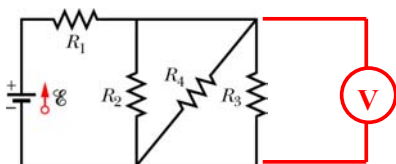- (b) Find the current in each resistor.

First note that $i_2 R_2 = i_3 R_3 = i_4 R_4$.



$$\begin{aligned} V &= iR_{234} \\ &= .050 \text{ A} \times 19\Omega \\ &= 0.95 \text{ V} \end{aligned}$$

$$\text{So } i_2 = V / R_2 = .95 / 50 = 19 \text{ mA}$$

$$i_3 = V / R_3 = .95 / 50 = 19 \text{ mA}$$

$$i_4 = V / R_4 = .95 / 75 = 12 \text{ mA}$$

Check: These three add up to $i_1 = 50 \text{ mA}$.


Q.27-2

$$R_2 = 2\Omega$$

$$R_3 = 3\Omega$$


$$i_2 = 6 \text{ A}$$

$$i_3 = ?$$

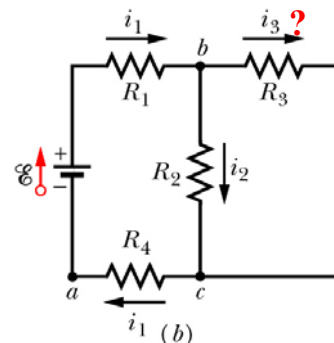

Calculate i_3 , find the closest single-digit number (0-9).

Q.27-2

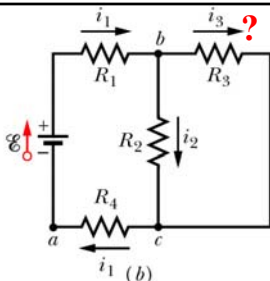

$$R_2 = 2\Omega$$

$$R_3 = 3\Omega$$

$$i_2 = 6 \text{ A}$$

$$i_3 = ?$$


- 1) 1 A
- 2) 2 A
- 3) 3 A
- 4) 4 A
- 5) 5 A
- 6) 6 A
- 7) 7 A
- 8) 8 A
- 9) 9 A

Q.27-2

$$R_2 = 2\Omega$$

$$R_3 = 3\Omega$$

$$i_2 = 6 \text{ A}$$

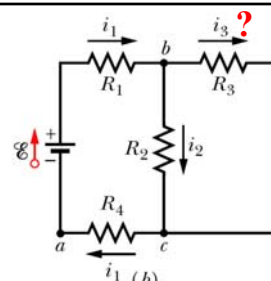

$$V_b - V_c = i_2 R_2 = i_3 R_3$$

$$\therefore i_3 = \frac{i_2 R_2}{R_3} = \frac{2}{3} i_2 = 4 \text{ A}$$

4

More Complicated Circuits

How do we solve a problem with more than one emf and several loops? We can't do it just by series and parallel resistor combinations.




Rules for Multiloop Circuits

- The net voltage change around any loop is zero.
"Energy conservation"
- The net current into any junction is zero.
"Charge conservation"


Using these two rules we can always get enough equations to solve for the currents if we are given the emfs and resistances.

Example

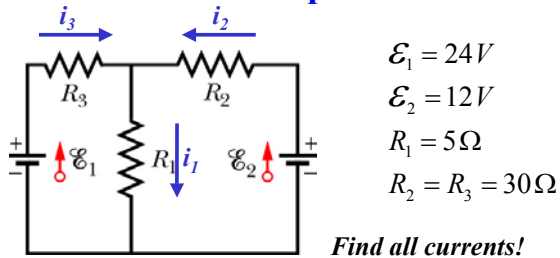

First define unknowns: i_1, i_2, i_3

Example (continued)

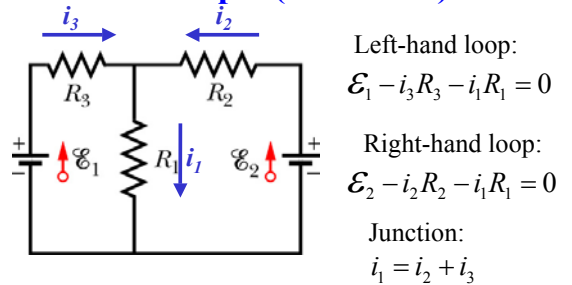

Algebra: solve 3 equations for 3 unknowns i_1, i_2, i_3

Loop and junction equations:

$$\mathcal{E}_1 - i_3 R_3 - i_1 R_1 = 0 \quad i_1 = i_2 + i_3$$

$$\mathcal{E}_2 - i_2 R_2 - i_1 R_1 = 0$$

Put in the given numbers and also replace i_1 by $i_2 + i_3$:

$$5i_1 + 30i_3 = 5i_2 + 35i_3 = 24$$


$$5i_1 + 30i_2 = 35i_2 + 5i_3 = 12$$

Solve two equations in two unknowns to get:


$$i_2 = 250 \text{ mA} \quad i_3 = 650 \text{ mA}$$

Add to get $i_1 = i_2 + i_3 = 900 \text{ mA}$

Check by using outer loop:

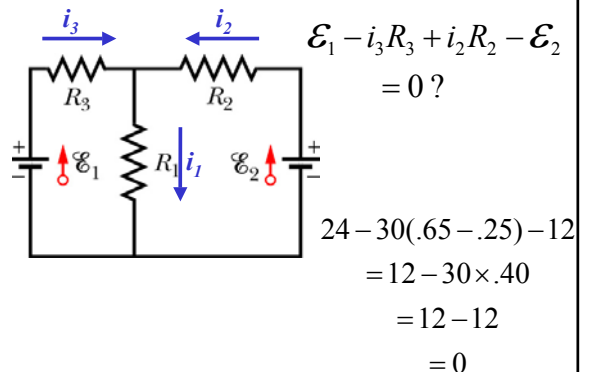

Repeat with a different R_1

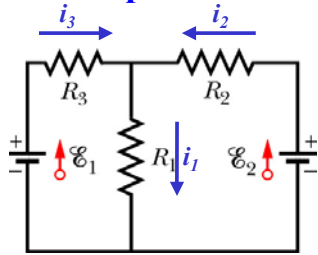



$$\begin{aligned} \mathcal{E}_1 &= 24V \\ \mathcal{E}_2 &= 12V \\ R_1 &= 40\Omega \\ R_2 = R_3 &= 30\Omega \end{aligned}$$

Exercise for the student: Same equations give **negative i_2** in this case! This means **current going downward** through right-hand battery.


Back to Basics

- Examples that don't involve so much algebra, but focus on the ideas of current and voltage.
- Even though you have a multiloop circuit so you need to write down the equations from the loop rule and the junction rule, you may not have to actually solve simultaneous equations.

Simpler Examples

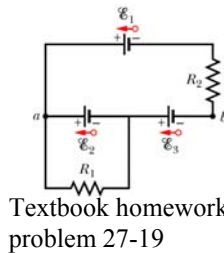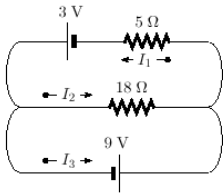

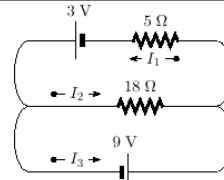Both these problems can be solved for **one unknown at a time**, without messy algebra.




$$\begin{aligned} 9 + 18 \times I_2 &= 0 & I_2 &= -0.5 A \\ 9 - 5 \times I_1 + 3 &= 0 & I_1 &= \frac{12}{5} = 2.4 A \\ I_3 &= I_1 - I_2 = 2.9 A \end{aligned}$$

Check:

$$P_{in} = 9I_3 + 3I_1 = 33.3 W \quad P_{out} = 5I_1^2 + 18I_2^2 = 33.3 W$$

Discharging a Capacitor

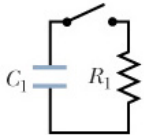

Capacitor has charge Q_0 .
At time $t=0$, close switch.
What is charge $q(t)$ for $t>0$?

Obviously $q(t)$ is a function which decreases gradually, approaching zero as t approaches infinity.



What function would do this?

$$q(t) = Q_0 e^{-t/\tau}$$

But what is the **time constant τ** ?

Analyze circuit equation: find $\tau = RC$

Charging a Capacitor

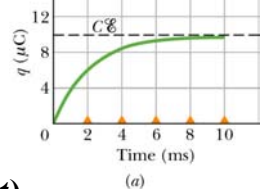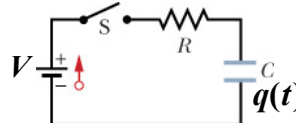


For small t , $q=0$ and $i=V/R$.

For large t , $q=CV$ and $i=0$.

$$q(t) = CV \left[1 - e^{-t/\tau} \right]$$

$$\tau = RC$$

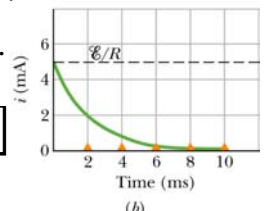

DC Circuits

- Resistance Review
- Following the potential around a circuit
- Multiloop Circuits
- RC Circuits

Homework for today:

Read Chapters 26, 27

Chapter 26 Questions 1, 3, 10

Chapter 26 Problems 1, 17, 18, 35, 77

Homework for tomorrow:

Chapter 27 Questions 1, 3, 5

Chapter 27 Problems 7, 19, 49

WileyPlus assignment: Chapters 26, 27

Exam #1

