

DC Circuits II

- Circuits Review
- RC Circuits
- Exponential growth and decay

Quiz Tomorrow on Chapters 26, 27

DC Circuits II

- Circuits Review
- RC Circuits
- Exponential growth and decay

Quiz Tomorrow on Chapters 26, 27

Circuits review so far


- Resistance and resistivity $R = \rho l / A$
- Ohm's Law and voltage drops $\Delta V = -iR$
- Power and Joule heating $P = iV$
- Resistors in series and parallel
- Loop and junction rules

Review: Series and Parallel Resistors

Series:

$$R = R_1 + R_2 + R_3$$


Why?

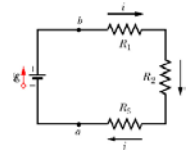

Parallel:

$$1/R = 1/R_1 + 1/R_2 + 1/R_3$$

Why?

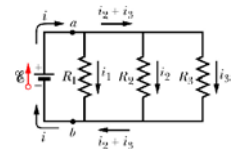


Review: Rules for Multiloop Circuits

- The net voltage change around any loop is zero.
"Energy conservation"
- The net current into any junction is zero.
"Charge conservation"

Using these two rules we can always get enough equations to solve for the currents if we are given the emfs and resistances.

Review example

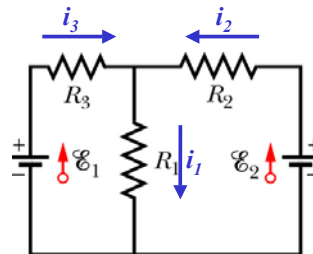

Left-hand loop:

$$\mathcal{E}_1 - i_3 R_3 - i_1 R_1 = 0$$

Right-hand loop:

$$\mathcal{E}_2 - i_2 R_2 - i_1 R_1 = 0$$



Junction:

$$i_1 = i_2 + i_3$$

Algebra: solve 3 equations for 3 unknowns i_1, i_2, i_3

If any $i < 0$, current flows the opposite direction.

Simpler Examples

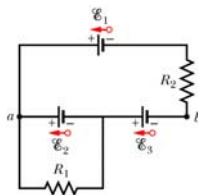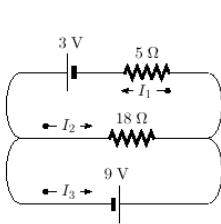

Textbook homework problem 27-19


Both these problems can be solved for *one unknown at a time*, without messy algebra.

Q.27-3

Resistors R_1 and R_2 are connected in series. If $R_2 > R_1$, what can you say about the resistance R of the combination?

1. $R > R_2$
2. $R_2 > R > R_1$
3. $R_1 > R$
4. None of the above

20

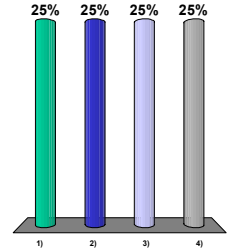

Q.27-3

- Resistors R_1 and R_2 are connected in series.
- $R_2 > R_1$.
- What can you say about the resistance R of this combination?

Solution:


$$R = R_1 + R_2 \quad \text{so} \quad R > R_2$$

- (1) $R > R_2$ (2) $R_2 > R > R_1$
 (3) $R_1 > R$ (4) None of the above

Q.27-4

Resistors R_1 and R_2 are connected in parallel. If $R_2 > R_1$, what can you say about the resistance R of the combination?

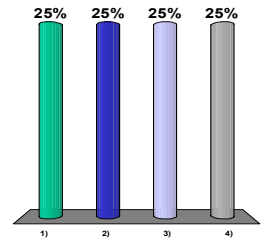1. $R > R_2$
2. $R_2 > R > R_1$
3. $R_1 > R$
4. None of the above




Q.27-4

- Resistors R_1 and R_2 are connected in parallel.
- $R_2 > R_1$.
- What can you say about the resistance R of this combination?

Solution: $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} \quad \text{so} \quad \frac{1}{R} > \frac{1}{R_1}$

- (1) $R > R_2$ (2) $R_2 > R > R_1$
 (3) $R_1 > R$ (4) None of the above

Discharging a Capacitor

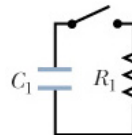

Capacitor has charge Q_0 .
 At time $t=0$, close switch.
 What is charge $q(t)$ for $t > 0$?

Obviously $q(t)$ is a function which decreases gradually, approaching zero as t approaches infinity.


What function would do this?

$$q(t) = Q_0 e^{-t/\tau}$$

But what is the time constant τ ?

Analyze circuit equation: find $\tau = RC$

Discharging a Capacitor

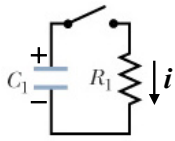

Sum voltage changes around loop:

$$Q/C - iR = 0, i = \frac{Q}{RC}$$



But

$$i = -\frac{dQ}{dt} \quad \text{Get differential equation for } Q(t): \quad \frac{dQ}{dt} = -\frac{Q}{RC}$$

Solution: $Q(t) = Q_0 e^{-t/\tau}$

Where τ is the time constant $\tau = RC$


Charging a Capacitor

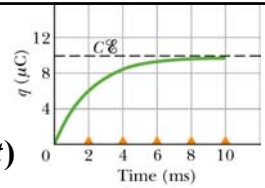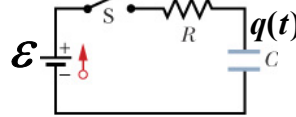

(a)

For small t, $q=0$ and $i = \varepsilon / R$
For large t, $i=0$ and $q = C\varepsilon$

But what are $q(t), i(t)$?

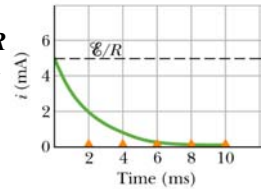

(b)

Charging a Capacitor


Sum voltage changes:

$$\varepsilon - iR - Q/C = 0$$

$$i = \frac{dQ}{dt} \quad \text{Get diff. eq.:} \quad \frac{dQ}{dt} = \frac{\varepsilon}{R} - \frac{Q}{RC}$$

Solution $Q(t) = C\varepsilon \left(1 - e^{-t/\tau}\right)$

$$\tau = RC$$

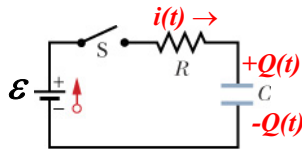


Charging a Capacitor

See solution gives desired behavior:


$$Q(t) = C\varepsilon \left(1 - e^{-t/\tau}\right)$$

$$\rightarrow 0 \quad \text{as } t \rightarrow 0$$
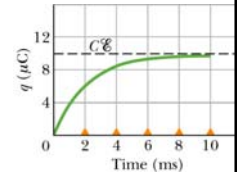
$$\rightarrow C\varepsilon \quad \text{as } t \rightarrow \infty$$



(a)

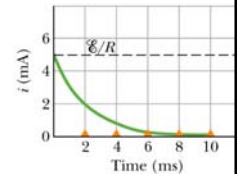

(b)

Exponential Growth and Decay

This *simple differential equation* occurs in many situations:

$$\frac{dQ}{dt} = (\text{Const.})Q$$

If $dQ/dt = +KQ$, we have the “snowball” equation: growth rate proportional to size. *Population growth.*


$$\frac{dQ}{dt} = +KQ \quad \longrightarrow \quad Q = Q_0 e^{+Kt}$$

If $dQ/dt = -KQ$, we have rate of *decrease* proportional to size. For example *radioactive decay.*

$$\frac{dQ}{dt} = -KQ \quad \longrightarrow \quad Q = Q_0 e^{-Kt}$$

Try Exponential Solution

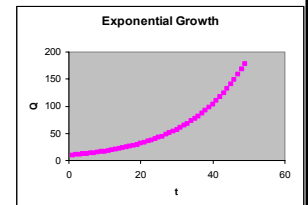We know we want a result which increases faster and faster. One function which does this is the exponential function. So try that:



To solve $\frac{dQ}{dt} = KQ$ try $Q(t) = Q_0 e^{t/\tau}$

Questions:

1. Is this a solution?
2. If so, what is the “time constant” τ ?

To solve $\frac{dQ}{dt} = KQ$ try $Q(t) = Q_0 e^{t/\tau}$

$$Q(t) = Q_0 e^{t/\tau}$$

$$\frac{dQ}{dt} = Q_0 \frac{d}{dt} e^{t/\tau} = \frac{Q_0}{\tau} e^{t/\tau} = \frac{Q}{\tau}$$

But we want $\frac{dQ}{dt} = KQ$

So we DO have a solution IF $\tau = 1/K$

Doubling Time

If $Q(t) = Q_0 e^{t/\tau}$
how long does it take for Q to double?

$$\frac{Q(t + \Delta t)}{Q(t)} = \frac{e^{(t+\Delta t)/\tau}}{e^{t/\tau}} = e^{\Delta t/\tau}$$

And $e^{\Delta t/\tau} = 2$ if $\Delta t/\tau = \ln(2) = 0.693$

So $\Delta t \cong 0.7\tau$

Radioactive Decay

For an unstable isotope, a certain fraction of the atoms will disintegrate per unit time.

For $\frac{dQ}{dt} = -KQ$ use $Q(t) = Q_0 e^{-t/\tau}$

Now τ is called the mean life, and the half-life is $T_{1/2} = \tau \ln(2) =$ time for half the remaining atoms to disintegrate, and

$$T_{1/2} \cong 0.7\tau$$

Discharge of a Capacitor

Back to electricity. From the loop rule we got

$$\frac{dQ}{dt} = -\frac{Q}{RC} = -KQ$$

So the solution is $Q(t) = Q_0 e^{-t/\tau}$

But what are Q_0 and τ ?

Initial condition: $Q_0 = Q(0)$

Time constant: $\tau = 1/K = RC$

Example

A 40 pF capacitor with a charge of 20 nC is discharged through a 50 MΩ resistor.

(a) What is the time constant?

$$\tau = RC = 40 \times 10^{-12} \times 50 \times 10^6 = 2.0 \times 10^{-3} \text{ s}$$

(b) At what time will 1/2 the charge remain?

$$T_{1/2} = 0.7\tau = 0.7 \times 2.0 \times 10^{-3} \text{ s} = 1.4 \text{ ms}$$

(c) How much charge will remain after 5 ms?

$$Q(t) = Q_0 e^{-t/\tau} = 20 \times e^{-2.5} = 1.64 \text{ nC}$$

Circuits Summary

Things to remember about DC circuits:

- Resistance and resistivity $R = \rho l / A$
- Ohm's Law and voltage drops $\Delta V = -iR$
- Power and Joule heating $P = iV$
- Resistors in series and parallel
- Loop and junction rules
- RC circuits: charging and discharging a capacitor
- RC time constant $Q(t) = Q_0 e^{-t/\tau}$ $\tau = RC$

Quiz tomorrow on Chapters 26,27.