

## Oscillating Currents

- Ch.30: Induced E Fields: Faraday's Law
- Ch.30: RL Circuits
- Ch.31: Oscillations and AC Circuits

## Review: Inductance

• If the current through a coil of wire changes, there is an induced emf proportional to the rate of change of the current.


• Define the proportionality constant to be the *inductance L*:

$$\mathcal{E} = -L \frac{di}{dt}$$


• SI unit of inductance is the **henry (H)**.
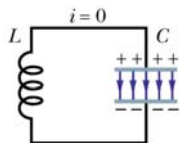
## LC Circuit Oscillations

Suppose we try to discharge a capacitor, using an *inductor* instead of a resistor:



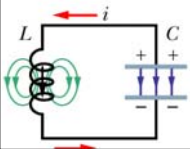At time  $t=0$  the capacitor has maximum charge and the current is zero.




Later, current is increasing and capacitor's charge is decreasing

## Oscillations (cont'd)

What happens when  $q=0$ ?

Does  $I=0$  also?

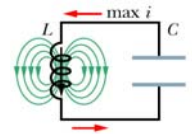
No, because inductor does not allow sudden changes.



In fact,  $q = 0$  means  $i = \text{maximum!}$

So now, charge starts to build up on C again, but in the *opposite direction!*


Textbook Figure 31-1

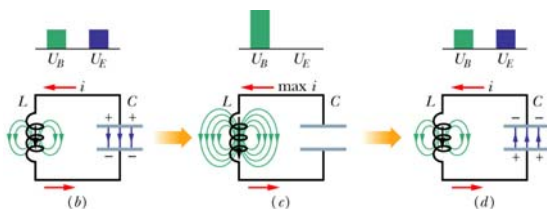

Energy is moving back and forth between C,L

$$U_L = U_B = \frac{1}{2} Li^2 \quad U_C = U_E = \frac{1}{2} q^2 / C$$

Textbook Figure 31-1

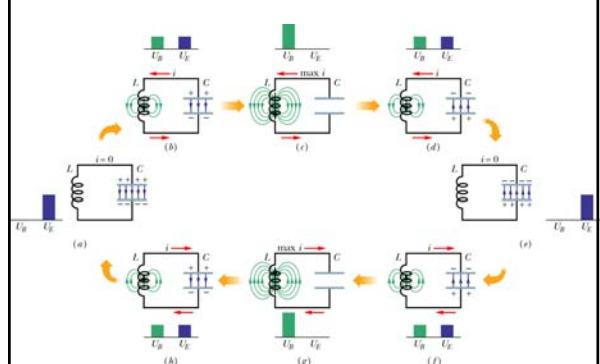

## Mechanical Analogy

- Looks like SHM (Ch. 15) Mass on spring.
- Variable  $q$  is like  $x$ , distortion of spring.
- Then  $i=dq/dt$ , like  $v=dx/dt$ , velocity of mass.


By analogy with SHM, we can guess that

$$q = Q \cos(\omega t)$$

$$i = \frac{dq}{dt} = -\omega Q \sin(\omega t)$$
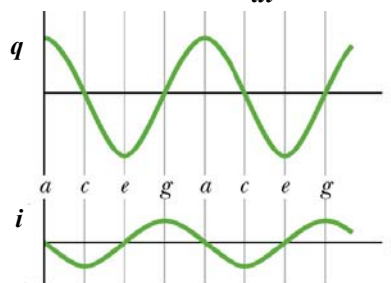
## Look at Guessed Solution

$$q = Q \cos(\omega t) \quad i = \frac{dq}{dt} = -\omega Q \sin(\omega t)$$



## Mathematical description of oscillations


Note essential terminology:

*amplitude, phase, frequency, period, angular frequency.* You **MUST** know what these words mean! If necessary review Chapters 10, 15.

## Get Equation by Loop Rule

If we go with the current as shown, the loop rule gives:

$$-\frac{q}{C} - L \frac{di}{dt} = 0$$

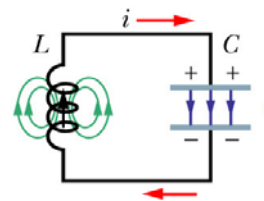

Now replace  $i$  by  $dq/dt$  to get:

$$\frac{d^2q}{dt^2} = -\left(\frac{1}{LC}\right)q$$

## Guess Satisfies Equation!

Start with  $q = Q \cos(\omega t)$   
 so that  $\frac{dq}{dt} = -\omega Q \sin(\omega t)$   $\frac{d^2q}{dt^2} = -\left(\frac{1}{LC}\right)q$

And taking one more derivative gives us

$$\frac{d^2q}{dt^2} = -\omega^2 Q \cos(\omega t) = -\omega^2 q$$

So the solution is correct, provided our angular frequency satisfies

$$\omega^2 = \left(\frac{1}{LC}\right)$$

## LC Circuit Example

Given an inductor with  $L = 8.0$  mH and a capacitor with  $C = 2.0$  nF, having initial charge  $q(0) = 50$  nC and initial current  $i(0) = 0$ .

- What is the frequency of oscillations (in Hz)?
- What is the maximum current in the inductor?
- What is the capacitor's charge at  $t = 30 \mu\text{s}$ ?

### Example: Part (a)

$$L = 8 \text{ mH}, C = 2 \text{ nF}, q(0) = 50 \text{ nC}, i(0) = 0$$

(a) What is the frequency of the oscillations?

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{8 \times 10^{-3} \times 2 \times 10^{-9}}} = 2.5 \times 10^5 \frac{\text{rad}}{\text{s}}$$

$$f = \frac{\omega}{2\pi} = \frac{2.5 \times 10^5 \text{ rad/s}}{6.28 \text{ rad/cycle}} = 4 \times 10^4 = \underline{40 \text{ kHz}}$$

### Example: Part (b)

$$(L = 8 \text{ mH}, C = 2 \text{ nF}, q(0) = 50 \text{ nC}, i(0) = 0)$$

(b) What is the maximum current?

$$E = \frac{Q^2}{2C} = \frac{(50 \times 10^{-9})^2}{2 \times 2.0 \times 10^{-9}} = 6.25 \times 10^{-7} \text{ J}$$

$$\text{But } E = \frac{1}{2} LI^2 \quad \text{so} \quad I^2 = \frac{2E}{L}$$

$$\text{So } I = \sqrt{\frac{2E}{L}} = \sqrt{\frac{2 \times 6.25 \times 10^{-7}}{8 \times 10^{-3}}} = \underline{12.5 \text{ mA}}$$

### Example: Part (c)

$$(L = 8 \text{ mH}, C = 2 \text{ nF}, q(0) = 50 \text{ nC}, i(0) = 0)$$

(c) What is the charge at  $t = 30 \mu\text{s}$ ?

$$\begin{aligned} q(t) &= Q \cos(\omega t) \\ &= (50 \text{ nC}) \cos(2.5 \times 10^5 \times 30 \times 10^{-6}) \\ &= (50 \text{ nC}) \cos(7.5 \text{ rad}) \\ &= (50 \text{ nC}) \cos(430^\circ) \\ &= 50 \times 0.347 = \underline{17 \text{ nC}} \end{aligned}$$

### AC Voltage Sources

- For an AC circuit, we need an *alternating emf*, or AC power supply.
- This is characterized by its *amplitude and its frequency*.



$$\mathcal{E} = \mathcal{E}_m \sin \omega t$$

← amplitude      ← angular frequency


### Notation for oscillating functions



Note that the textbook uses *lower-case* letters for oscillating **time-dependent** voltages and currents, with *upper-case* letters for the corresponding **amplitudes**.

$$v = V \sin \omega t \quad i = I \sin \omega t$$

### AC Currents and Voltages

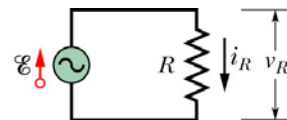

$$\mathcal{E} = \mathcal{E}_m \sin \omega t = v_R = V_R \sin \omega t$$

Ohm's Law gives:  $i_R = v_R / R = (\mathcal{E}_m / R) \sin \omega t$

So the AC current is:  $i_R = I_R \sin \omega t$

So the amplitudes are related by:  $\underline{V_R = I_R R}$


## AC Voltage-Current Relations

- First apply an alternating emf to a resistor, a capacitor, and an inductor *separately*, before dealing with them all at once.
- For  $C, L$ , define *reactance*  $X$  analogous to resistance  $R$  for resistor. Measured in ohms.

$$\begin{aligned} V_R &= I_R R \\ V_C &= I_C X_C \\ V_L &= I_L X_L \end{aligned}$$

## Summary for R, C, L Separately

“ELI the ICE man”

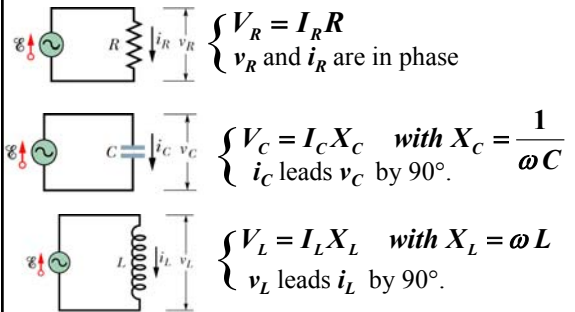

### Q.31-1

Which of the following is true about the phase relation between the current and the voltage for an inductor?

- The current is in phase with the voltage.
- The current is ahead of the voltage by  $90^\circ$ .
- The current is behind the voltage by  $90^\circ$ .
- They are out of phase by  $180^\circ$ .

### Q.31-1

Which of the following is true about the phase relation between the current and the voltage for an inductor?

Remember ELI the ICE man!

Inductor: voltage leads current.

- The current is in phase with the voltage.
- The current is ahead of the voltage by  $90^\circ$ .
- The current is behind the voltage by  $90^\circ$ .
- They are out of phase by  $180^\circ$ .


### Q.31-1

What is the phase relation between the current and the voltage for an inductor?

Proof:


$$\text{Let } i = I \sin(\omega t)$$
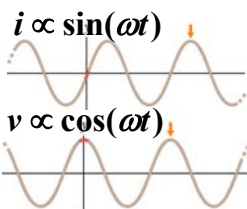
$$\text{Drop is } v = L \frac{di}{dt} = LI\omega \cos(\omega t)$$



$v$  hits peak before  $i$

### Q.31-2

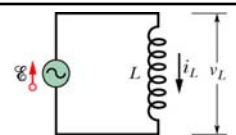

An inductor  $L$  carries a current with amplitude  $I$  at angular frequency  $\omega$ . What is the amplitude  $V$  of the voltage across this inductor?

$$\begin{aligned} I &= 3.0 \text{ A} \\ \omega &= 200 \text{ rad/s} \\ L &= .03 \text{ H} \end{aligned}$$

- $V_L = 0.5 \text{ V}$
- $V_L = 2.0 \text{ V}$
- $V_L = 6.0 \text{ V}$
- $V_L = 12 \text{ V}$
- $V_L = 18 \text{ V}$
- $V_L = 600 \text{ V}$


### Q.31-2

The **reactance** is:

$$X_L = \omega L = 200 \times .03 = 6.0 \Omega$$

Thus the **voltage amplitude** is:
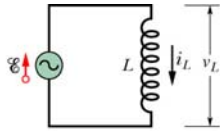
$$V_L = I_L X_L = 3.0 A \times 6.0 \Omega = 18 V$$



$$I = 3.0 A$$

$$\omega = 200 \text{ rad/s}$$

$$L = .03 H$$

- (1)  $V_L = 0.5 V$    (2)  $V_L = 2.0 V$    (3)  $V_L = 6.0 V$   
 (4)  $V_L = 12 V$    (5)  $V_L = 18 V$    (6)  $V_L = 600 V$

### Impedance

The "AC Ohm's Law" is:  $\mathcal{E}_m = IZ$

where  $Z$  is called the **impedance**.

Obviously, for a resistor,  $Z = R$   
 for a capacitor  $Z = X_C$  and for an inductor  $Z = X_L$


But if you have a **combination** of circuit elements,  $Z$  is more complicated.

### Impedance and Phase Angle

General problem:  
 if we are given

$$\mathcal{E}(t) = \mathcal{E}_m \sin \omega t$$

can we find  $i(t)$ ?

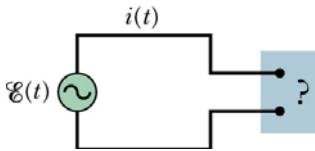


We can always write  $i(t) = I \sin(\omega t - \phi)$

By definition of impedance  $I = \mathcal{E}_m / Z$

Given  $\mathcal{E}_m$  and  $\omega$ , find  $Z$  and  $\phi$ .   ??
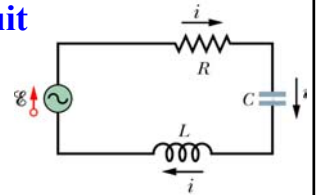
### Series RLC Circuit

- The currents are all equal.
- The voltage drops add up to the applied emf as a function of time:  $\mathcal{E} = v_R + v_C + v_L$



**BUT:** Because of the **phase differences**, the **amplitudes** do **not** add:  $\mathcal{E}_m \neq V_R + V_C + V_L$


So the impedance is not just a sum:  $Z \neq R + X_C + X_L$

### Results for series circuits

$$\mathcal{E}(t) = \mathcal{E}_m \sin \omega t$$

$$i(t) = I \sin(\omega t - \phi)$$

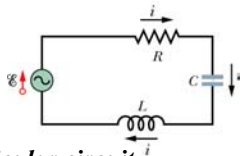It turns out that for **this particular circuit**




$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$
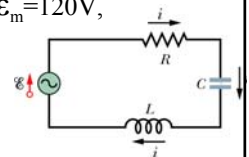
### Series Circuit Example

Given  $L = 50 \text{ mH}$ ,  $C = 60 \mu\text{F}$ ,  $\mathcal{E}_m = 120 \text{ V}$ ,  
 $f = 60 \text{ Hz}$ , and  $I = 4.0 \text{ A}$ .

- What is the impedance?
- What is the resistance  $R$ ?



Solution to (a) is easy:

$$Z = \frac{\mathcal{E}_m}{I} = \frac{120}{4} = \underline{30 \Omega}$$

### Example (part b)

$$(a) Z = 30 \Omega$$

$$L = 50 \text{ mH}, C = 60 \mu\text{F}, \varepsilon_m = 120\text{V}, f = 60\text{Hz}, I = 4.0\text{A}$$

(b) What is the resistance  $R$ ?

$$\omega = 2\pi f = 2 \times 3.14 \times 60 = 377 \text{ rad / s}$$

$$X_L = \omega L = 377 \times 50 \times 10^{-3} = 18.8 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{377 \times 60 \times 10^{-6}} = 44.2 \Omega$$

$$X_C - X_L = 44.2 - 18.8 = 25.4 \Omega$$

$$R = \sqrt{Z^2 - (X_L - X_C)^2} = \sqrt{30^2 - 25.4^2} = \underline{16 \Omega}$$

### Oscillating Currents

- Ch.30: Induced E Fields: Faraday's Law
- Ch.30: RL Circuits
- Ch.31: Oscillations and AC Circuits
  
- Chapter 30 Homework for Today:
  - Questions 1, 3, 7
  - Problems 3, 5, 29, 44
- Chapter 31 Homework for Tomorrow:
  - Questions 3, 4, 7
  - Problems 5, 19, 39
- WileyPlus chapters 30, 31.